 


# Embedded Systems Design, Spring 2025

## Lecture 1



# Combinational Logic Design Principles

# About this course



- EMB2 – continuation of EMB1, stand alone course, 5 ECTS
- 8 Practice Assignments (not compulsory)
  - 8 during the semester (individual/groups of two) + 1 which is optional
  - You will get feedback on the 8 assignments: correct solutions (from your hand-ins)
- End of teaching period: A theory test for extra bonus points (10%)
- In June: written exam, 3 hours (theory + practical part)
- Structure of the course/topics may be adjusted during the semester, please follow itslearning for changes in schedule

# Course schedule

- Theory + labs (check schedule in itslearning)
- Theory sessions will be on :
  - Friday (MC) /
  - Thursday noon (EL + EIB)
- Support videos and tutorials in itslearning
- Labs will either be exercises or practical implementation
  - Designated rooms + use of the e-labs (Alsion e-lab, CIE e-lab)
- The first part of the semester will focus more on theory
- The second part of the semester will focus more on practice
  
# Contents

- Logic components
- Boolean algebra
- Latches and flip-flops
- State machines



**Book: Digital Design: Principles and Practices 4th Edition,**  
by [John F. Wakerly](#) (Author)

- Microcontroller hardware
- Peripherals / Serial communication
- Interrupts
- AD/DA conversion




# Entering the digital world

- We live in an analog world
- Digital logic – mapping the infinite set of real values to 0 and 1
- When talking about real circuits: 0 – **low**, 1 – **high**
- Noise immunity
- Buffer circuits

# Physical states in various cases

Technology	0	1
Pneumatic logic	Low pressure	High pressure
Relay logic	Circuit open	Circuit closed
CMOS logic	0 - 1.5V	3.5 - 5.0V
TTL	0 – 0.8V	2.0 – 5.0V
Dynamic memory	Capacitor discharged	Capacitor charged
Erasable memory	Electrons trapped	Electrons released
Microprocessor on-chip	Fuse blown	Fuse intact
Fiber optics	Light off	Light on
Magnetic tape	Flux direction north	Flux direction south
CD	No pit	Pit
CD – R	Dye in crystalline state	Dye in noncrystalline state

# Types of logic circuits

 

Combinational circuit: output depends on the input,  
operation described by a truth table.

Sequential circuit: output depends on input and previous inputs,  
operation described by a state table.


# Basic logic functions

*2-input AND gate*




A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

*2-input OR gate*

 

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

*NOT gate truth table*

 


Input	Output
0	1
1	0




# NAND, NOR

*2-input NAND gate*

 

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

*2-input NOR gate*

 


A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

*Equivalent gate circuit*



*Equivalent gate circuit*

 

# Logic families


- 1930: Bell Labs – relays
- 1940: Eniac – 18 000 vacuum tubes
- 1950 – 1960 – invention of the IC
- 1960 – Transistor - Transistor Logic (TTL, based bipolar transistors)
- 1960 – Metal-oxide semiconductor field effect (lower power consumption, slower)
- 1980 – Complementary MOS (CMOS) – increase in performance

# CMOS Logic

# Logic levels


**Figure 3-6**

 Logic levels for typical CMOS logic circuits.




# pMOS, nMOS

nMOS

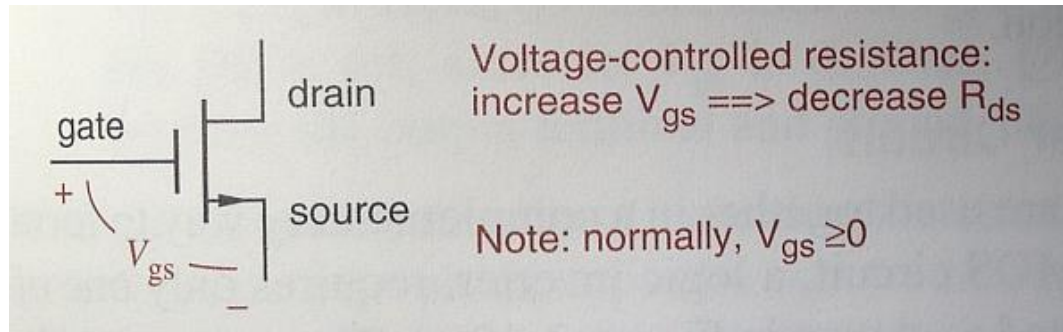

pMOS

 

# CMOS Inverter


**Figure 3-10**

CMOS inverter:

(a) circuit diagram;

(b) functional behavior;

(c) logic symbol.


 


(b)

$V_{IN}$	$Q1$	$Q2$	$V_{OUT}$
0.0 (L)	off	on	5.0 (H)
5.0 (H)	on	off	0.0 (L)


(c)



  

**Figure 3-11**  
Switch model for  
CMOS inverter: (a)  
LOW input; (b) HIGH  
input.

**Figure 3-12**  
CMOS inverter logical  
operation.

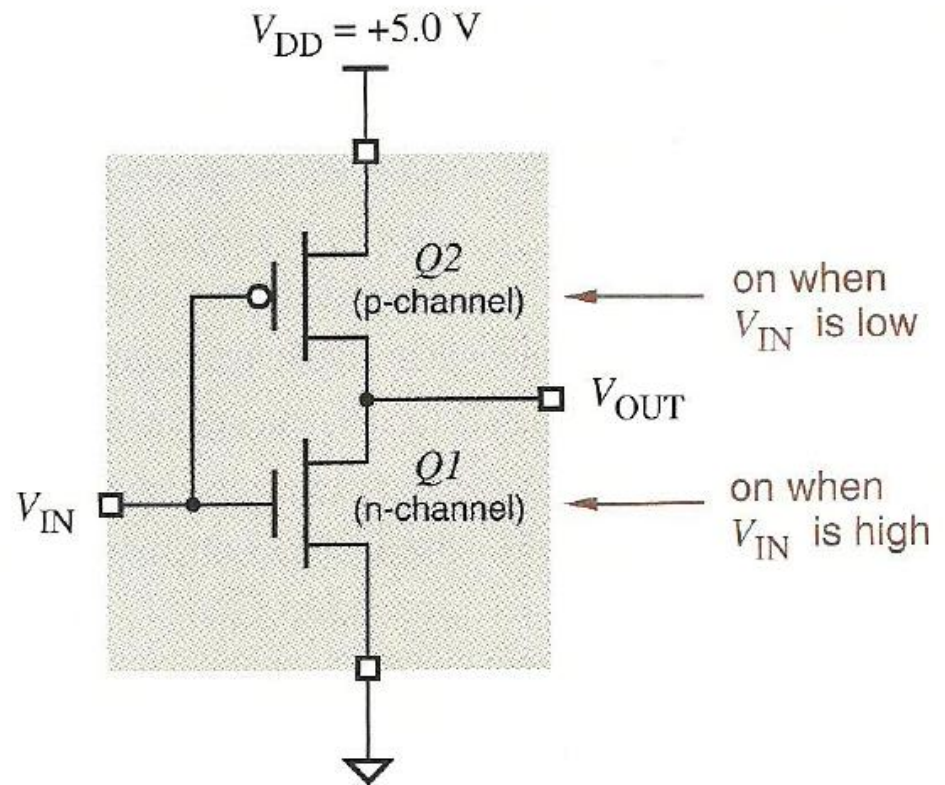




**Figure 3-13**

 CMOS 2-input  
NAND gate:

(a) circuit diagram;  
(b) function table;  
(c) logic symbol.




(b)


A	B	$Q1$	$Q2$	$Q3$	$Q4$	Z
L	L	off	on	off	on	H
L	H	off	on	on	off	H
H	L	on	off	off	on	H
H	H	on	off	on	off	L

(c)



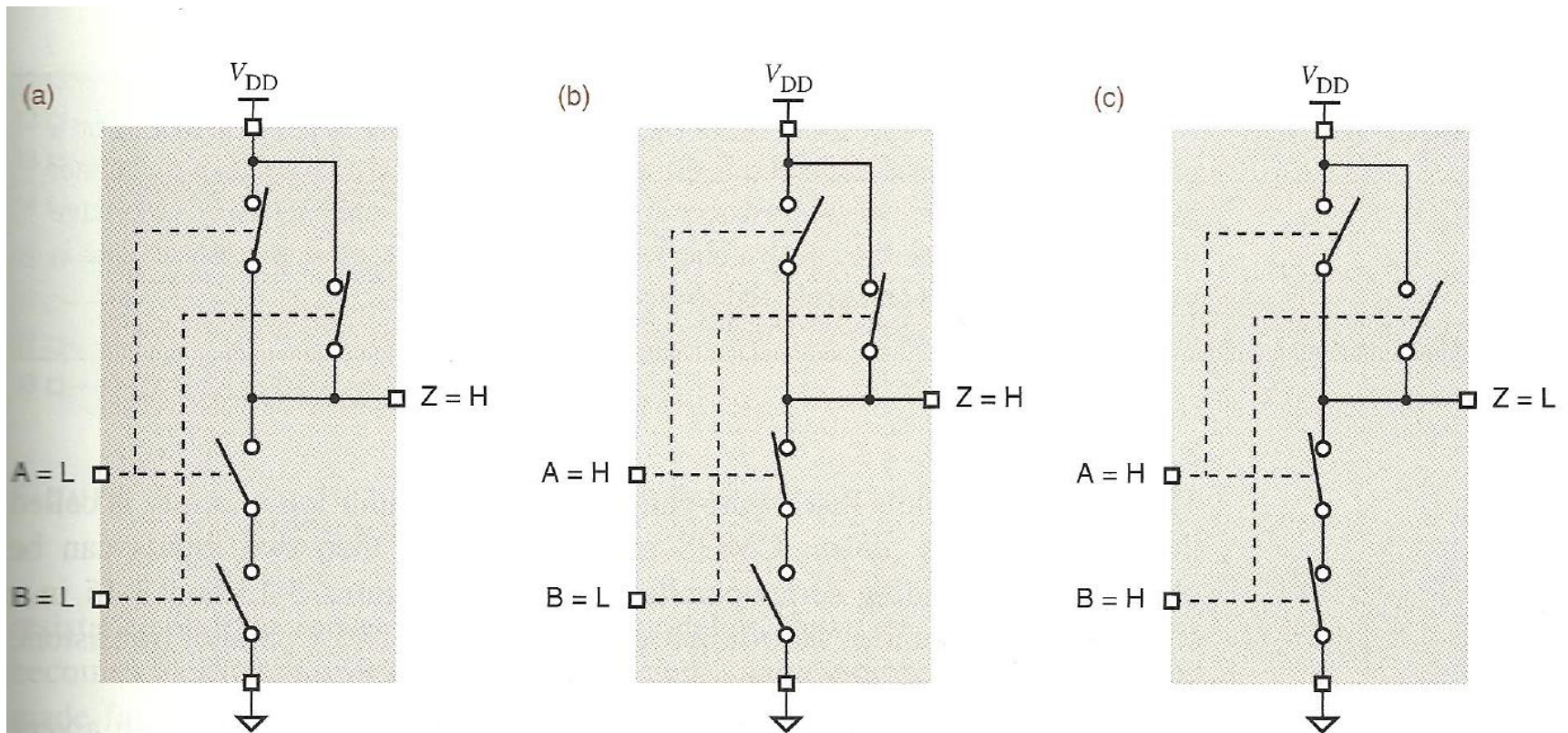

**Figure 3-14** Switch model for CMOS 2-input NAND gate: (a) both inputs LOW; (b) one input HIGH; (c) both inputs HIGH.

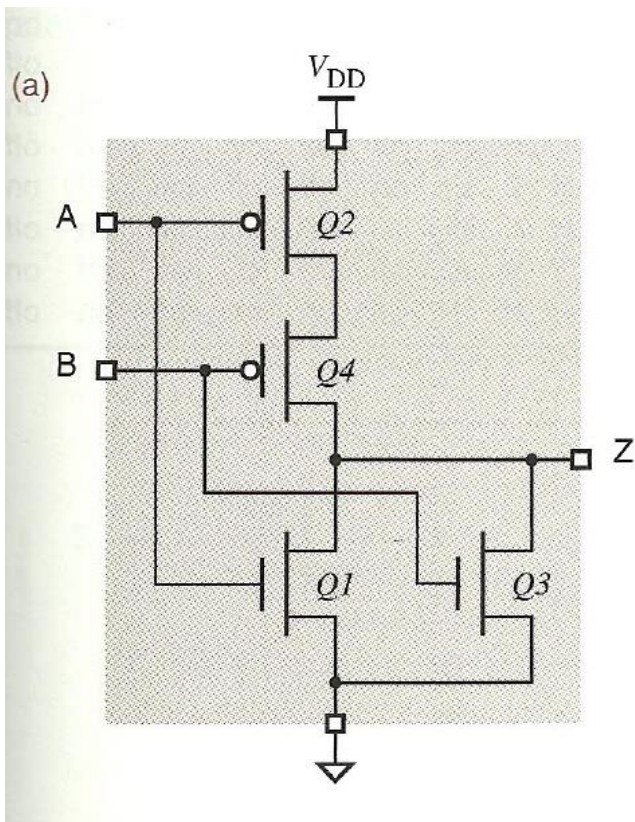


(b)

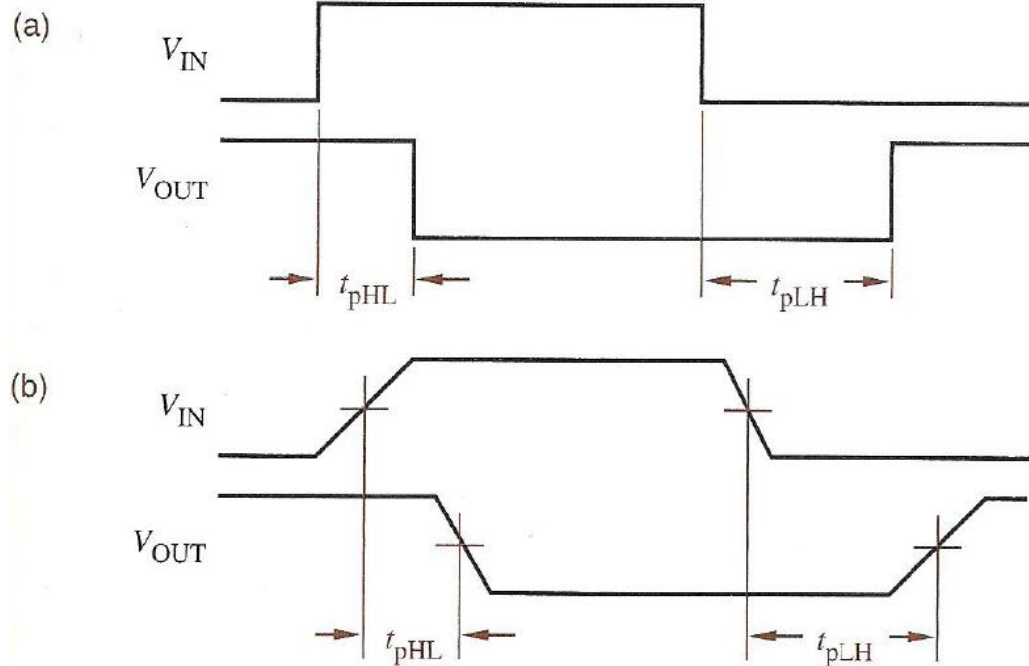A	B	$Q1$	$Q2$	$Q3$	$Q4$	Z
L	L	off	on	off	on	H
L	H	off	on	on	off	L
H	L	on	off	off	on	L
H	H	on	off	on	off	L

 


**Figure 3-15**  
CMOS 2-input  
NOR gate:  
(a) circuit diagram;  
(b) function table;  
(c) logic symbol.



**Figure 3-42**  
Propagation delays  
for a CMOS inverter:  
(a) ignoring rise and  
fall times; (b) measured at  
midpoints of transitions.

 





**Figure 3-48** Device operation with slowly changing inputs: (a) a noisy, slowly changing input; (b) output produced by an ordinary inverter; (c) output produced by an inverter with 0.8 V of hysteresis.

**Figure 3-47**

A Schmitt-trigger inverter: (a) input-output transfer characteristic; (b) logic symbol.




# Three state outputs

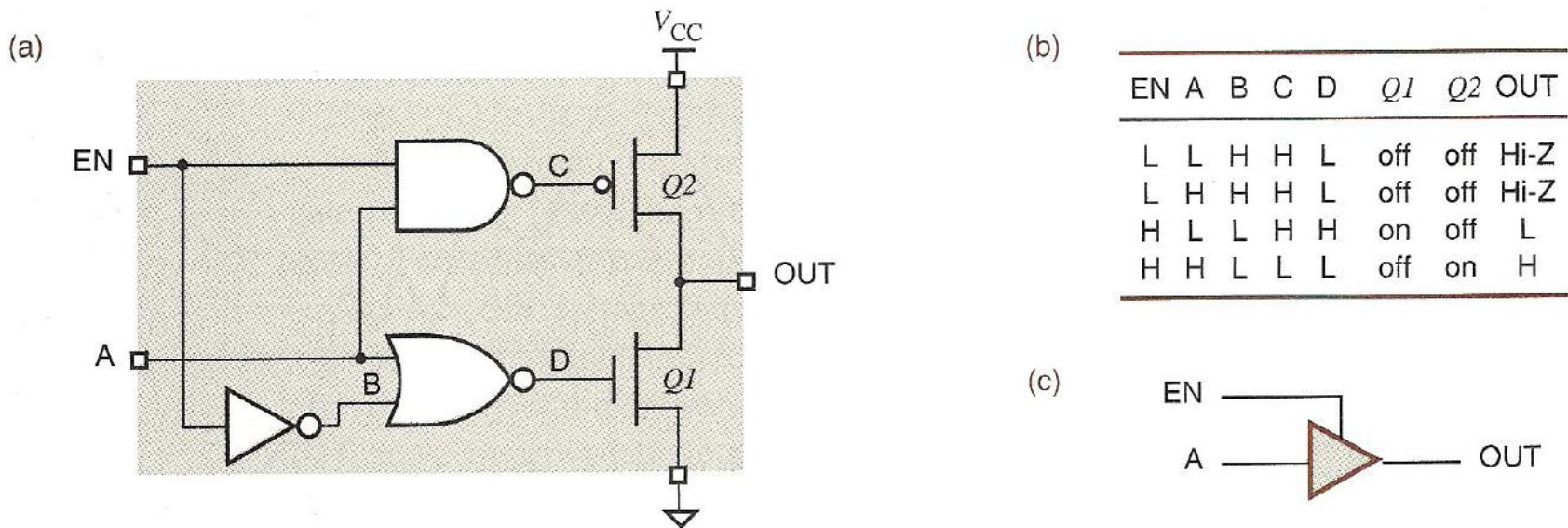


**Figure 3-49** CMOS three-state buffer: (a) circuit diagram; (b) function table; (c) logic symbol.

**Figure 3-50**  
Open-drain CMOS  
NAND gate: (a) circuit  
diagram; (b) function  
table; (c) logic symbol.

 


(b)

A	B	Q1	Q2	Z
L	L	off	off	open
L	H	off	on	open
H	L	on	off	open
H	H	on	on	L

 



**Figure 3-51**  
Open-drain CMOS  
NAND gate driving  
a load.

 

# Exercises

- $F = XY + X'Y'Z$
- $F = X + Y' + XYZ$
- $F = X'Y' + XY + Z'$
- $F = (X + Y'Z)' + X'YZ'$