 


# Embedded Systems Design, Spring 2025

## Lecture 3



## Sequential Logic: Latches and flip-flops



# Review from last time

- ?

# Bistability

**Figure 7-2**

  A pair of inverters forming a bistable element.




# Flip flops (latches)

- 1918 – Eccles - Jordan triggered circuit
- Latches can change their state at any time
- Flip-flops can change their state only when a clocking signal is changing

# Clock types



- Clock types

 

**Figure 7-1**  
Clock signals:  
(a) active high;  
(b) active low.

# S-R latch

- S-R latch:

  

(b)


S	R	Q	Q $\bar{N}$
0	0	last Q	last Q $\bar{N}$
0	1	0	1
1	0	1	0
1	1	0	0

**Figure 7-5**  
S-R latch: (a) circuit design using NOR gates; (b) function table.


# Typical operation

- *Metastable region*: when the output is unpredictable

**Figure 7-6** Typical operation of an S-R latch: (a) “normal” inputs; (b) S and R asserted simultaneously.

 

- *Propagation delay*: time need for an input signal change to generate an output signal change
- *Recovery time*: giving the minimum separation between S and R as to be not simultaneous

 


**Figure 7-8** Timing parameters for an S-R latch.



# $\overline{S}\text{-}\overline{R}$ latches


- $S'$  and  $R'$  are active low, therefore opposite operation

**Figure 7-9**  $\overline{S}\text{-}\overline{R}$  latch: (a) circuit design using NAND gates; (b) function table; (c) logic symbol.

 


(b) Function table:

$S_L$	$R_L$	$Q$	$QN$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	last Q	last QN

 


# $\overline{S}\text{-}\overline{R}$ latch with enable

- Why? To control when the inputs are active

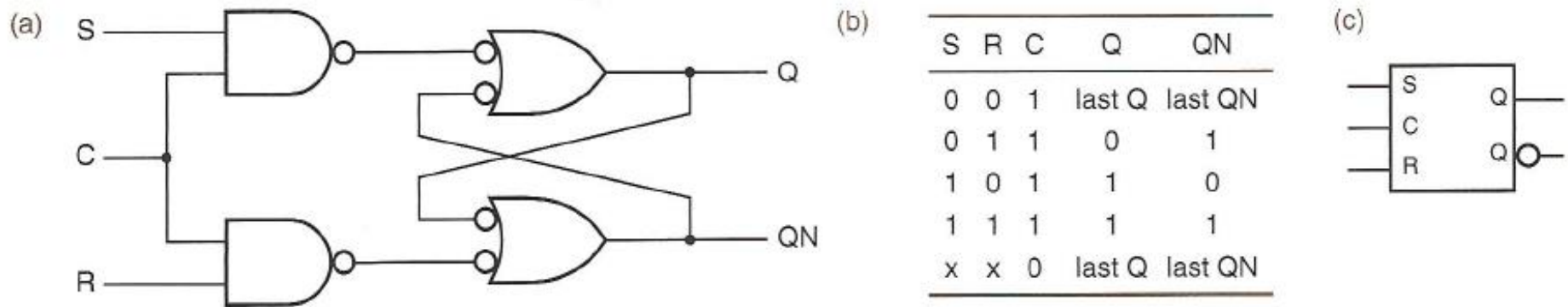


**Figure 7-10** S-R latch with enable: (a) circuit using NAND gates; (b) function table; (c) logic symbol.
 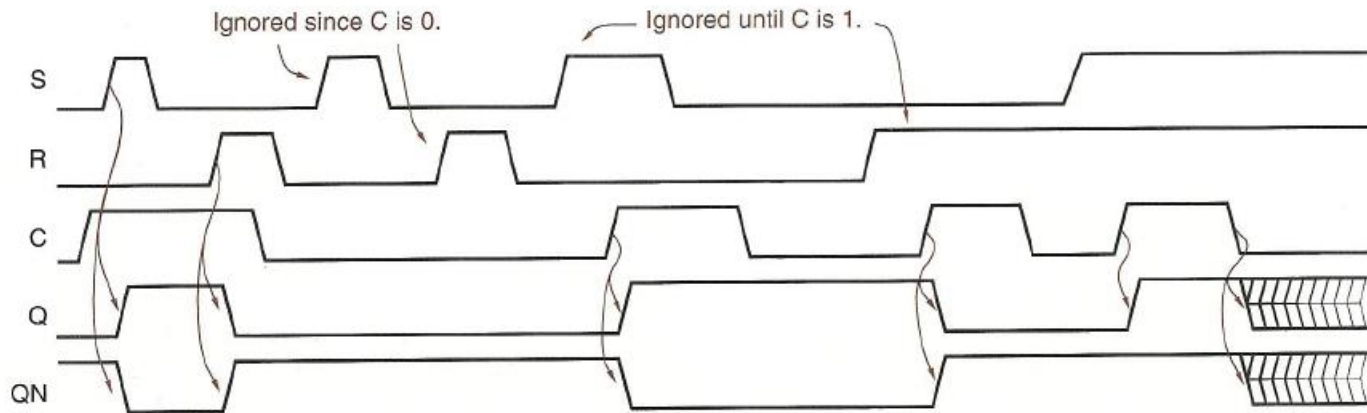
# Typical operation




**Figure 7-10** S-R latch with enable: (a) circuit using NAND gates; (b) function table; (c) logic symbol.


**Figure 7-11** Typical operation of an S-R latch with enable.



# D-latches

 


**Figure 7-12** D latch: (a) circuit design using NAND gates; (b) function table; (c) logic symbol.

 

**Figure 7-13** Functional behavior of a D latch for various inputs.

# Timing parameters


**Figure 7-14** Timing parameters for a D latch.

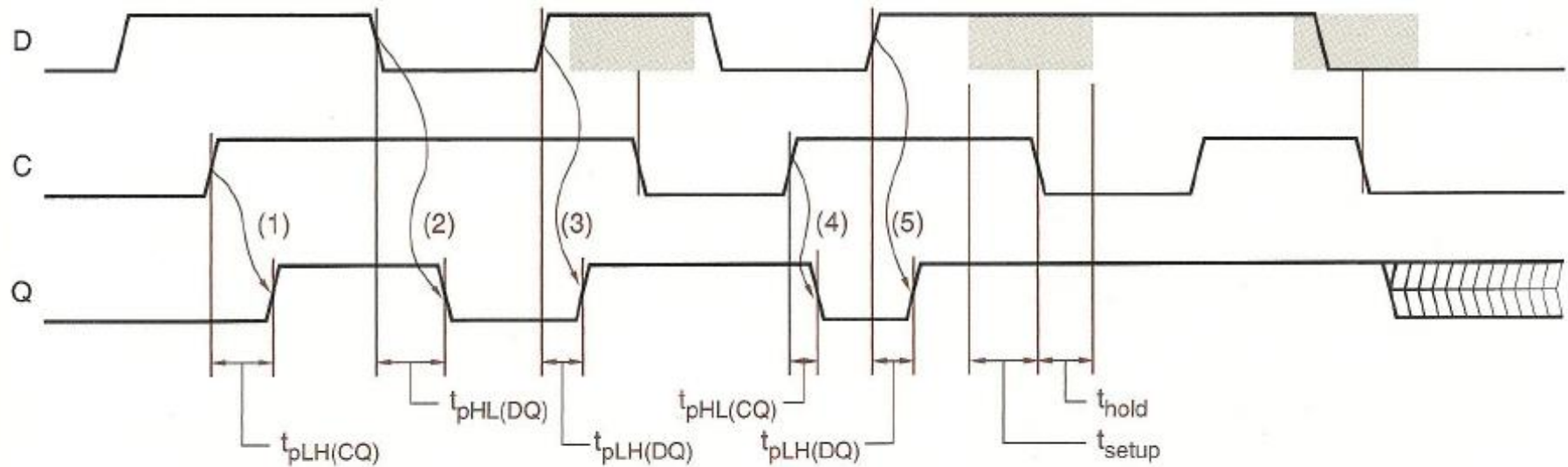



# Edge triggered D Flip Flop

- **Clk:** dynamic input indicator – edge triggered behavior

**Figure 7-15** Positive-edge-triggered D flip-flop: (a) circuit design using D latches; (b) function table; (c) logic symbol.

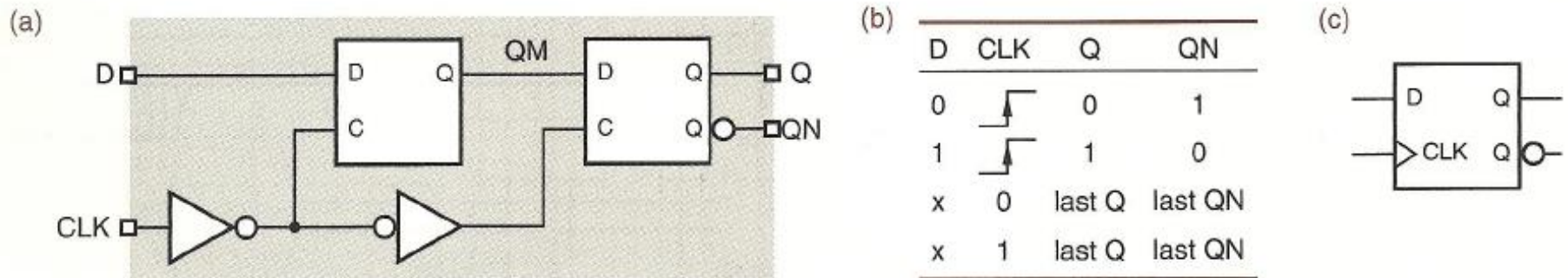


**Figure 7-15** Positive-edge-triggered D flip-flop: (a) circuit design using D latches; (b) function table; (c) logic symbol.

 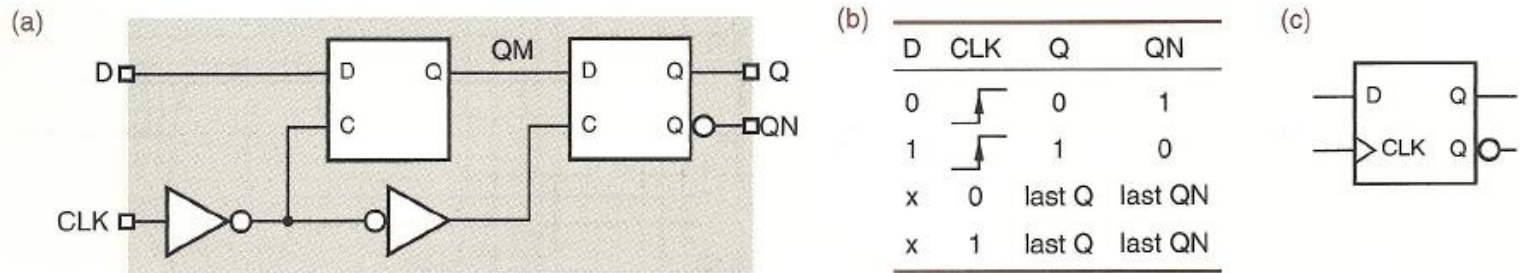


**Figure 7-16** Functional behavior of a positive-edge-triggered D flip-flop.



**Figure 7-15** Positive-edge-triggered D flip-flop: (a) circuit design using D latches; (b) function table; (c) logic symbol.

 


**Figure 7-17** Timing behavior of a positive-edge-triggered D flip-flop.

 



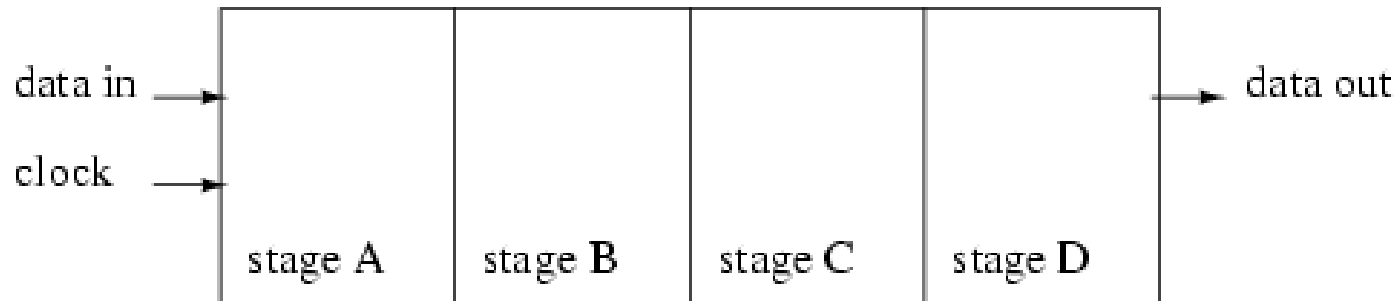
# Shift registers

- They produce a discrete delay for a specific digital signal. The delay is given by “n” stages.
- Conveyor belt similarity




Serial-in, serial-out shift register with 4-stages

# Shift registers

 


**Figure 8-37**  
Structure of a  
serial-in, serial-out  
shift register.

# Serial – in, parallel - out

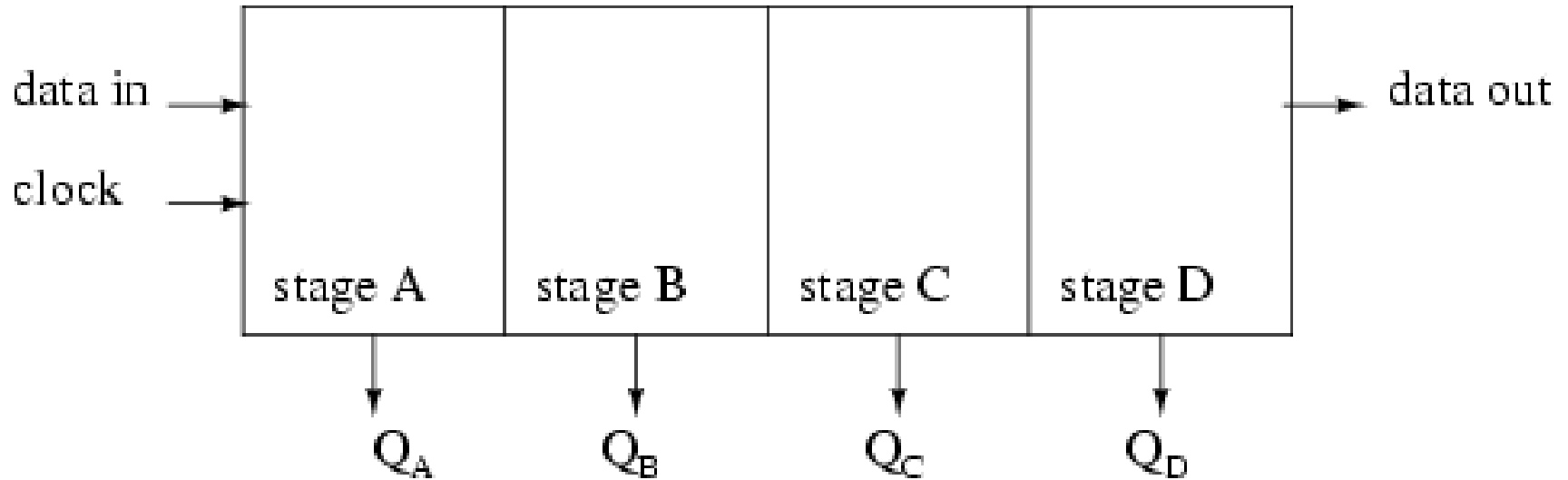


Serial-in, parallel-out shift register with 4-stages

**Figure 8-38**  
Structure of a  
serial-in, parallel-out  
shift register.

 


# Parallel - in, serial - out

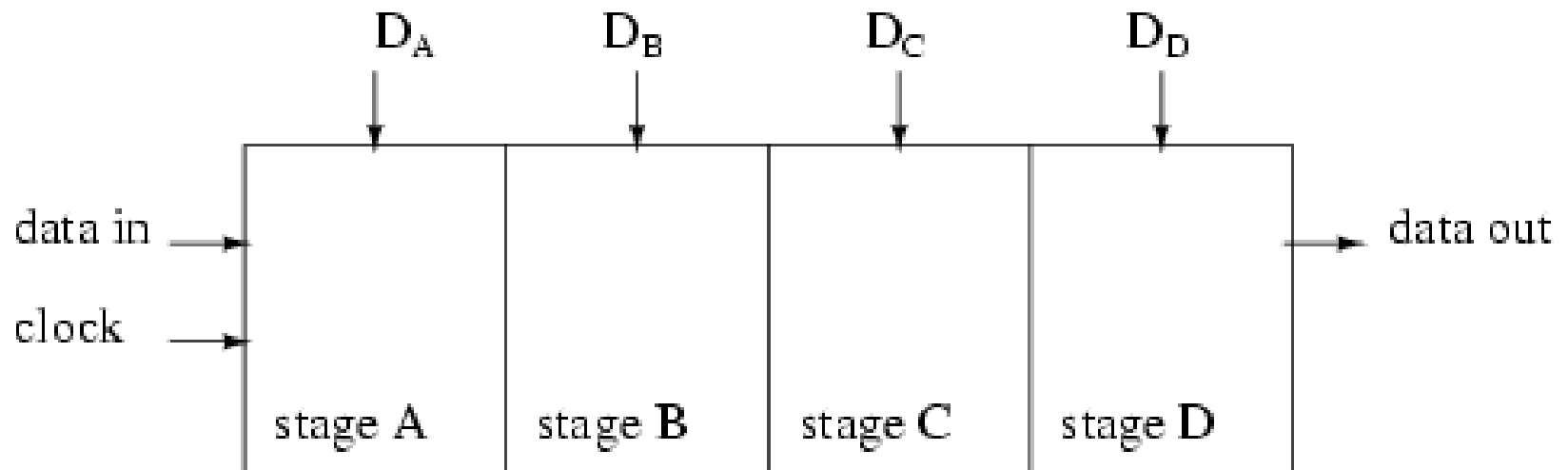


Parallel-in, serial-out shift register with 4-stages

# Parallel - in, serial - out

 


**Figure 8-39** Structure of a parallel-in, serial-out shift register.
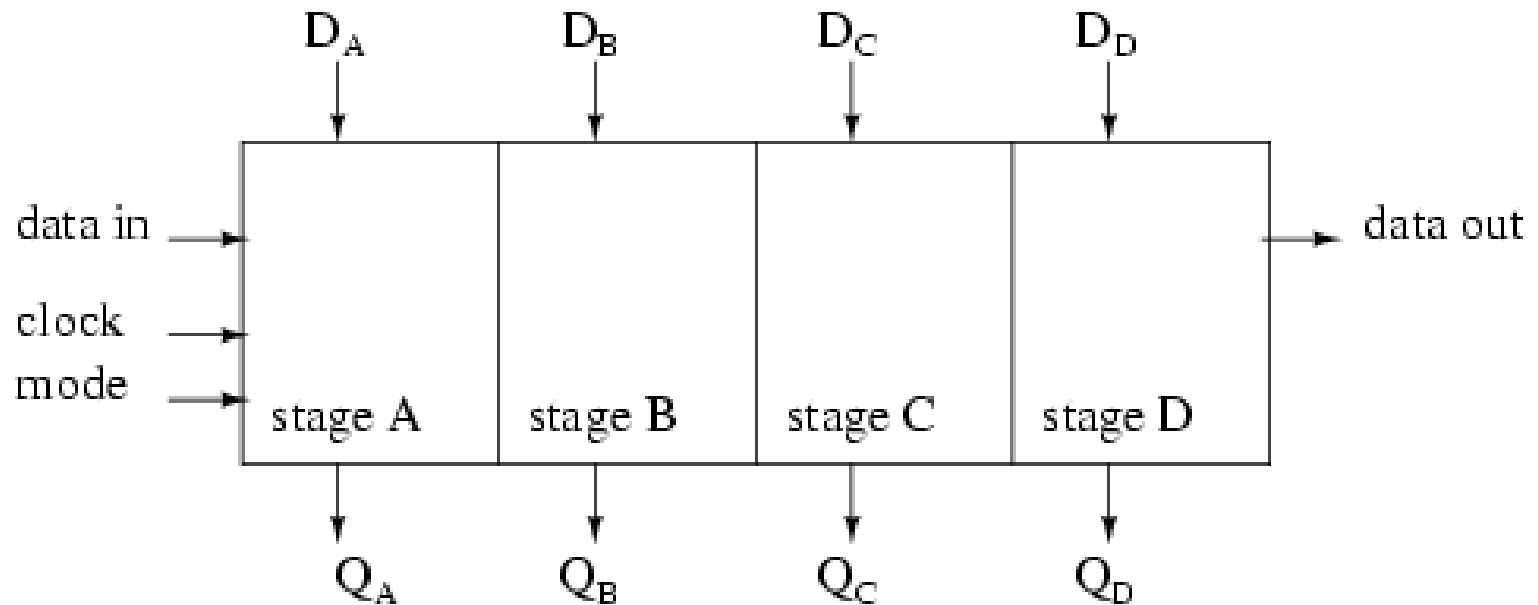
# Parallel – in, parallel - out



Parallel-in, parallel-out shift register with 4-stages

 

**Figure 8-40** Structure of a parallel-in, parallel-out shift register.



# Example: 74x194, 4 bit shift register

**Table 8-24**


Function table for the 74x194 4-bit universal shift register.

Function	Inputs		Next state			
	S1	S0	QA*	QB*	QC*	QD*
Hold	0	0	QA	QB	QC	QD
Shift right	0	1	RIN	QA	QB	QC
Shift left	1	0	QB	QC	QD	LIN
Load	1	1	A	B	C	D


Example:

S1:0

S0:1

 

## ■ Example

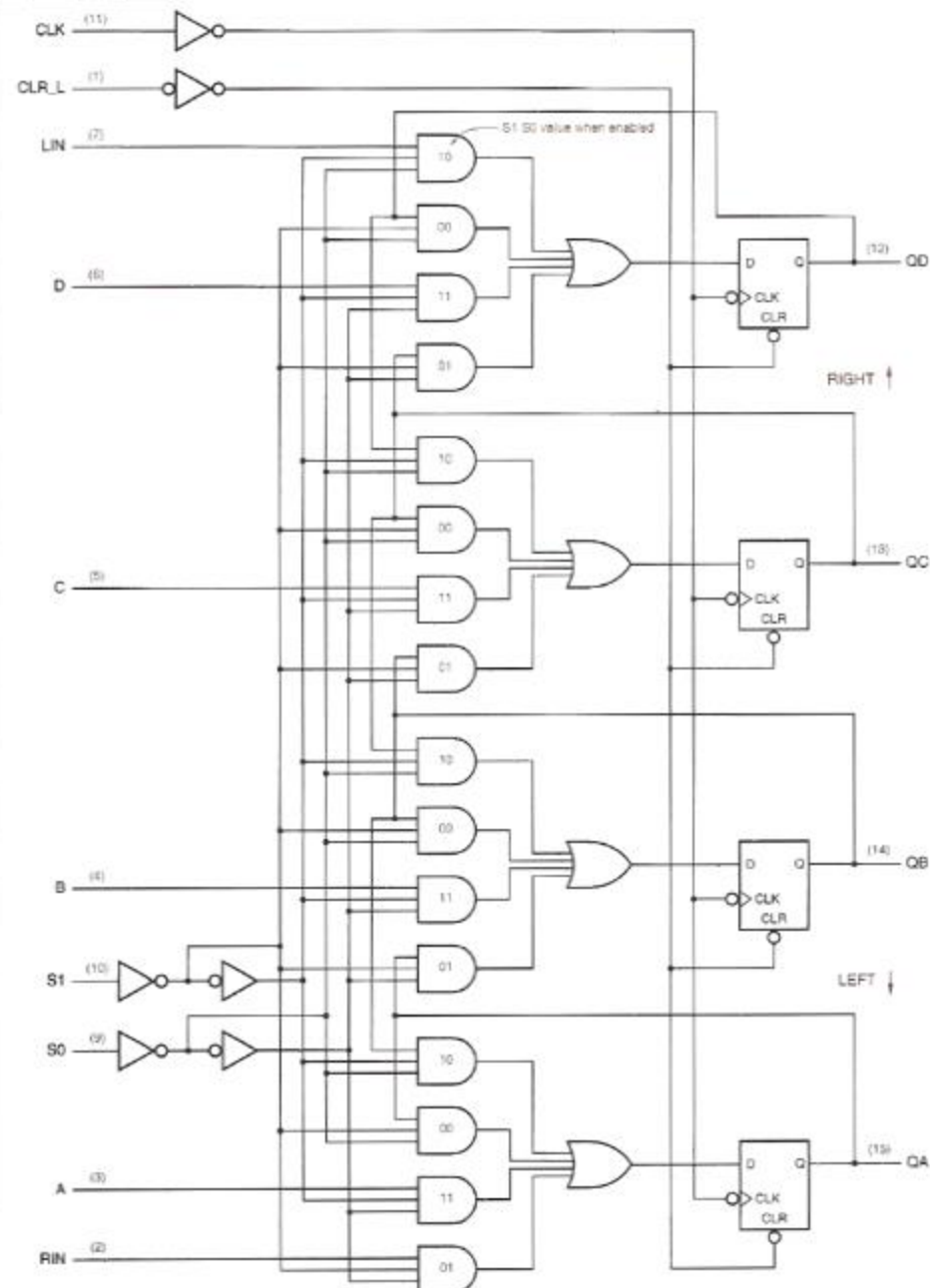

**Figure 8-41** Logic diagram for the 74x194 4-bit universal shift register, including pin numbers for a standard 16-pin dual in-line package.