 


Embedded Systems Design, Spring 2025

Lecture 2




Combinational Logic Design Principles

Review from last time

- ?

Types of logic circuits

 

Combinational circuit: output depends on the input,
operation described by a truth table.

Sequential circuit: output depends on input and previous inputs,
operation described by a state table.

Logic circuits

- **Circuit analysis:**
 - Start with a logic diagram
 - Formal description of the circuit:
 - Truth table
 - Logic expression
- **Circuit synthesis:**
 - Start with a formal description
 - Truth table
 - Logic expression
 - Continue with a logic diagram

Switching algebra


- George Boole, 1854 – invented boolean algebra
- Claude Shannon, 1938 – switching algebra (using relays)
 - Variable X could have two values: 0 or 1
- Positive logic convention (opposite for negative logic convention)
 - 0 – low voltage
 - 1 – high voltage
- Axioms:
 - basic definitions assumed to be true
 - Everything else can be derived from them

Axioms

Axiom	Relation	Axiom'	Relation
A1	$X = 0$ if $X \neq 1$	A1'	$X = 1$ if $X \neq 0$
A2	If $X = 0$, then $X' = 1$	A2'	If $X = 1$, then $X' = 0$


Figure 4-1

 Signal naming and algebraic notation for an inverter.



- X' is the same as $\neg X$, $\sim X$, \overline{X}

AND (\cdot), OR ($+$)

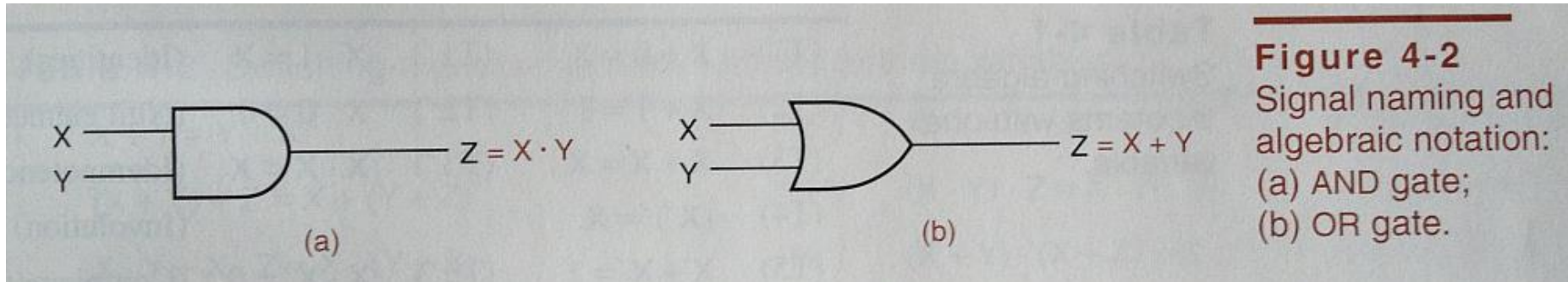

Axiom	Relation	Axiom'	Relation
A3	$0 \cdot 0 = 0$	A3'	$1 + 1 = 1$
A4	$1 \cdot 1 = 1$	A4'	$0 + 0 = 0$
A5	$0 \cdot 1 = 1 \cdot 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$

Single variable theorems

T	Relation	T	Relation	Name
T1	$X + 0 = X$	(T1)'	$X \cdot 1 = X$	Identities
T2	$X + 1 = 1$	(T2)'	$X \cdot 0 = 0$	Null elements
T3	$X + X = X$	(T3)'	$X \cdot X = X$	Idempotency
T4	$(X')' = X$	(T4)'		Involution
T5	$X + X' = 1$	(T5)'	$X \cdot X' = 0$	Complements

Multiple variable theorems





T	Relation	T	Relation	Name
T6	$X + Y = Y + X$	(T6)'	$X \cdot Y = Y \cdot X$	Commutativity
T7	$(X + Y) + Z = X + (Y + Z)$	(T7)'	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$	Associativity
T8	$X \cdot Y + X \cdot Z = X \cdot (Y + Z)$	(T8)'	$(X + Y) \cdot (X + Z) = X + Y \cdot Z$	Distributivity
T9	$X + X \cdot Y = X$	(T9)'	$X \cdot (X + Y) = X$	Covering
T10	$X \cdot Y + X \cdot Y' = X$	(T10)'	$(X + Y) \cdot (X + Y') = X$	Combining
T11	$X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$			Consensus
T11'	$(X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$			

More theorems

T	Relation	T	Relation	Name
T12	$X + X + \dots + X = X$			Generalized idemp.
T12'	$X \cdot X \cdot \dots \cdot X = X$			
T13	$(X_1 \cdot X_2 \cdot \dots \cdot X_n)' = X_1' + X_2' + \dots + X_n'$			DeMorgan's theorems
T13'	$(X_1 + X_2 + \dots + X_n)' = X_1' \cdot X_2' \cdot \dots \cdot X_n'$			
T14	$[F(X_1, X_2, \dots, X_n, +, \cdot)]' = F(X_1', X_2', \dots, X_n', \cdot, +)$			Generalized DeMorgan's th.
T15	$F(X_1, X_2, \dots, X_n) = X_1 \cdot F(1, X_2, \dots, X_n) + X_1' \cdot F(0, X_2, \dots, X_n)$			Shannon's expansion

DeMorgan's theorems in use:

Figure 4-3 Equivalent circuits according to DeMorgan's theorem T13:
(a) AND-NOT; (b) NOT-OR; (c) logic symbol for a NAND gate;
(d) equivalent symbol for a NAND gate.

    

DeMorgan's theorems in use:



 


Figure 4-4 Equivalent circuits according to DeMorgan's theorem T13':
(a) OR-NOT; (b) NOT-AND; (c) logic symbol for a NOR gate;
(d) equivalent symbol for a NOR gate.


Example 1:

 

X	Y	Z
LOW	LOW	LOW
LOW	HIGH	LOW
HIGH	LOW	LOW
HIGH	HIGH	HIGH

 

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

 


X	Y	Z
1	1	1
1	0	1
0	1	1
0	0	0


Figure 4-5 A “type-1” logic gate: (a) electrical function table; (b) logic function table and symbol with positive logic; (c) logic function table and symbol with negative logic.

Example 2


Figure 4-6 A “type-2” logic gate: (a) electrical function table; (b) logic function table and symbol with positive logic; (c) logic function table and symbol with negative logic.

 

X	Y	Z
LOW	LOW	LOW
LOW	HIGH	HIGH
HIGH	LOW	HIGH
HIGH	HIGH	HIGH

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

 

X	Y	Z
1	1	1
1	0	0
0	1	0
0	0	0

Duality


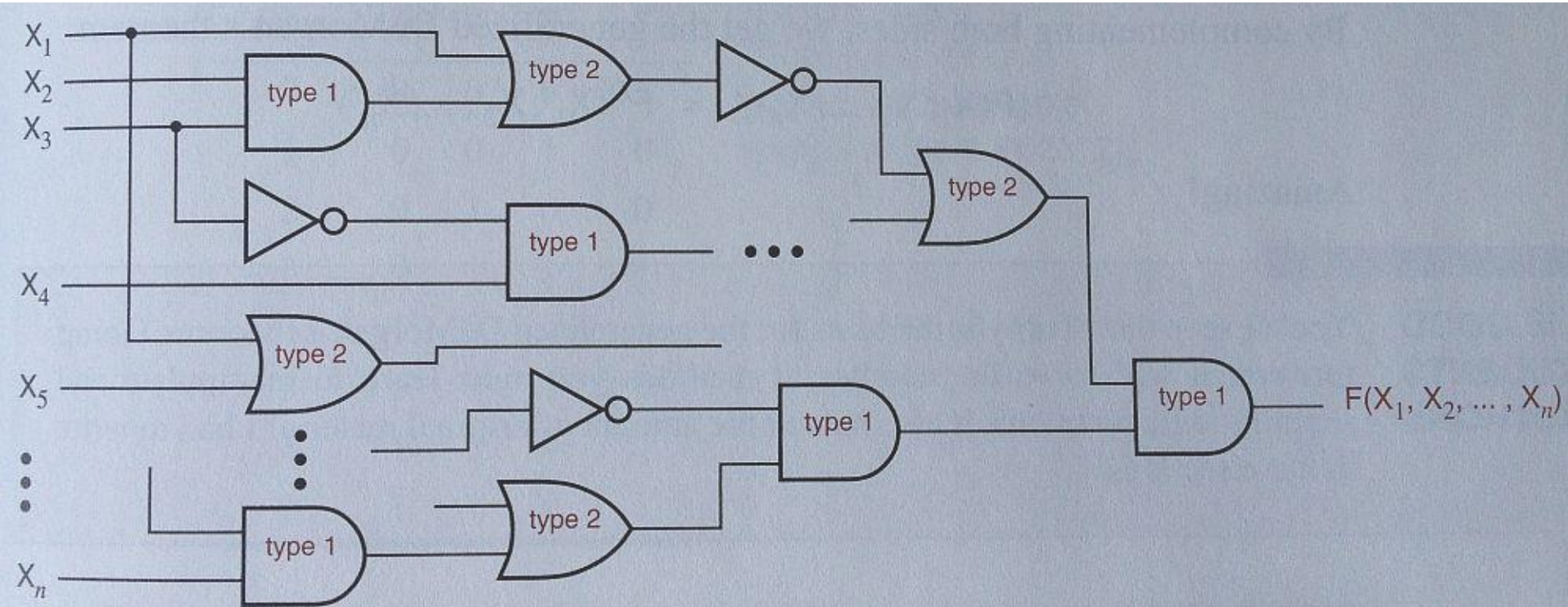


Figure 4-7 Circuit for a logic function using inverters and type-1 and type-2 gates under a positive-logic convention.

Duality

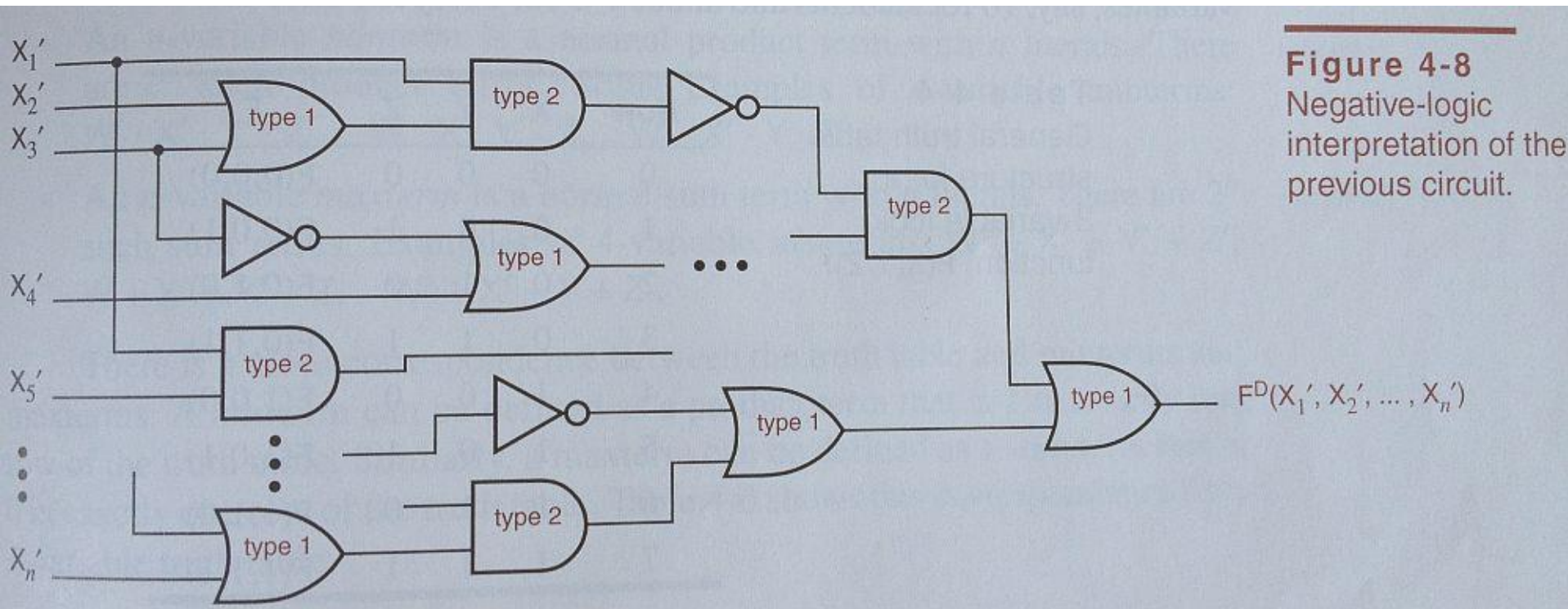

Representation of Logic Functions

- Truth tables

<i>Row</i>	X	Y	Z	F
0	0	0	0	F(0,0,0)
1	0	0	1	F(0,0,1)
2	0	1	0	F(0,1,0)
3	0	1	1	F(0,1,1)
4	1	0	0	F(1,0,0)
5	1	0	1	F(1,0,1)
6	1	1	0	F(1,1,0)
7	1	1	1	F(1,1,1)

In general: $F(X, Y, Z)$

<i>Row</i>	X	Y	Z	F
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

Particular logic function

Naming

- *A literal* – a variable or its complement; X, X', Y, Y'
- *A product term*: single literal or logical product:
 - $X, W \cdot X \cdot Y', W' \cdot Y'$
- *A sum term*: single literal or logical product:
 - $X', W+X+Y', W'+Y'$
- *Sum of products* and *product of sums*
- *Normal term* – a product or sum, where each variable appears only once
 - Ex: $W \cdot X \cdot Y', W+X'+Y'$
- *N-variable minterm* – a product with n literals:
 - Ex: 4-variables minterm: $W \cdot X \cdot Y' \cdot Z'$
- *N-variable maxterm* – a sum with n literals:
 - Ex: 4-variables maxterm: $W+X+Y+Z'$

Canonical sum and product

- Canonical sum** – a sum of the minterms corresponding to the table rows for which the output is 1
 - $F = \sum_{X,Y,Z} (0,3,4,6,7)$ – minterm list
 - $F = X'Y'Z' + X'YZ + XY'Z' + XYZ' + XYZ$
 - 0
3
4
6
7
- Canonical product** – a product of the maxterms corresponding to the table rows for which the output is 0
 - $F = \prod_{X,Y,Z} (1,2,5)$ – maxterm list
 - $(X+Y+Z')(X+Y'+Z)(X'+Y+Z')$
 - 1
2
5

Row	X	Y	Z	F
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1


Combinational Circuit Analysis + Synthesis

- Analysis
 - Determine the behavior for different inputs
 - Find the logic equation and compute a truth table
- Synthesis
 - Formal description of its function
 - Suggest different circuit structures
 - Transform into a standard form available
 - Sum of products: used in PLA
 - Truth table -> lookup memory in FPGA

Example – Analyzing this circuit

Figure 4-9


A 3-input, 1-output logic circuit.

 

- Start to build the truth table
- Z will take a series of values: 0, 1, 0, 1, 0, 1, 0, 1
- Y will take a series of values: 0, 0, 1, 1, 0, 0, 1, 1
- X will take a series of values: 0, 0, 0, 0, 1, 1, 1, 1
- **EXERCISE: Determine the output for this circuit!**


Solution

Figure 4-10 Gate outputs created by all input combinations.

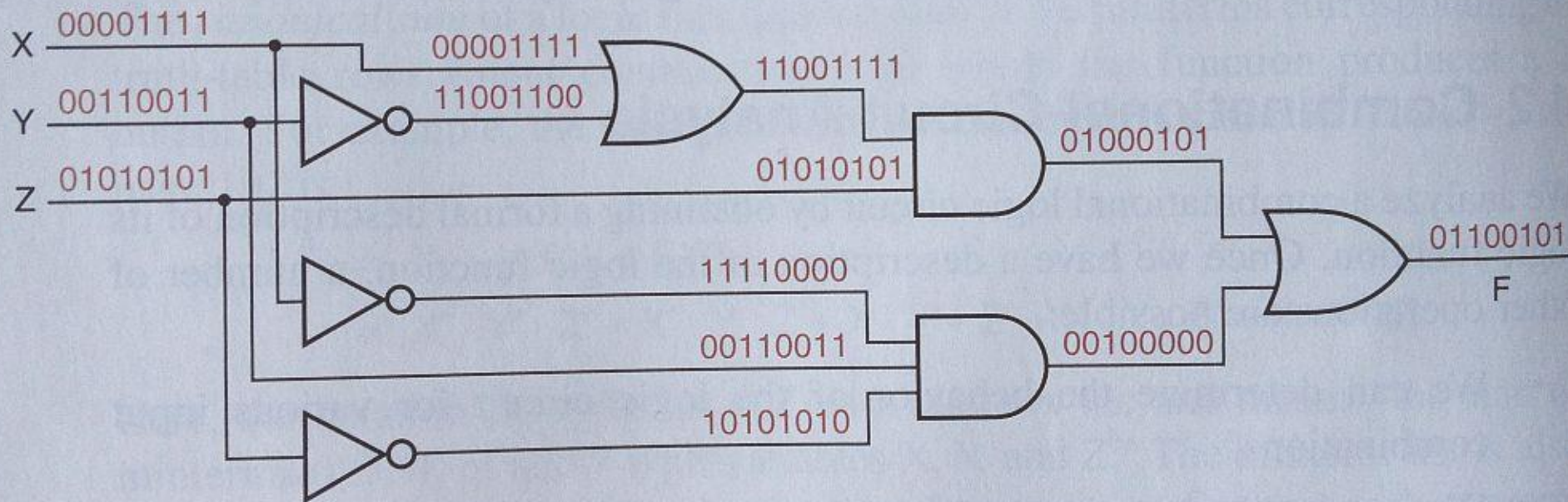


Secondary approach

Figure 4-9
A 3-input, 1-output
logic circuit.

 

- Use algebraic rules
 - Build up a paranthesized logic expression from the structure of the circuit
 - Start at the inputs, go towards outputs
 - Simplifying can be done (or not)
- **EXERCISE: Write the output function!**

Solution

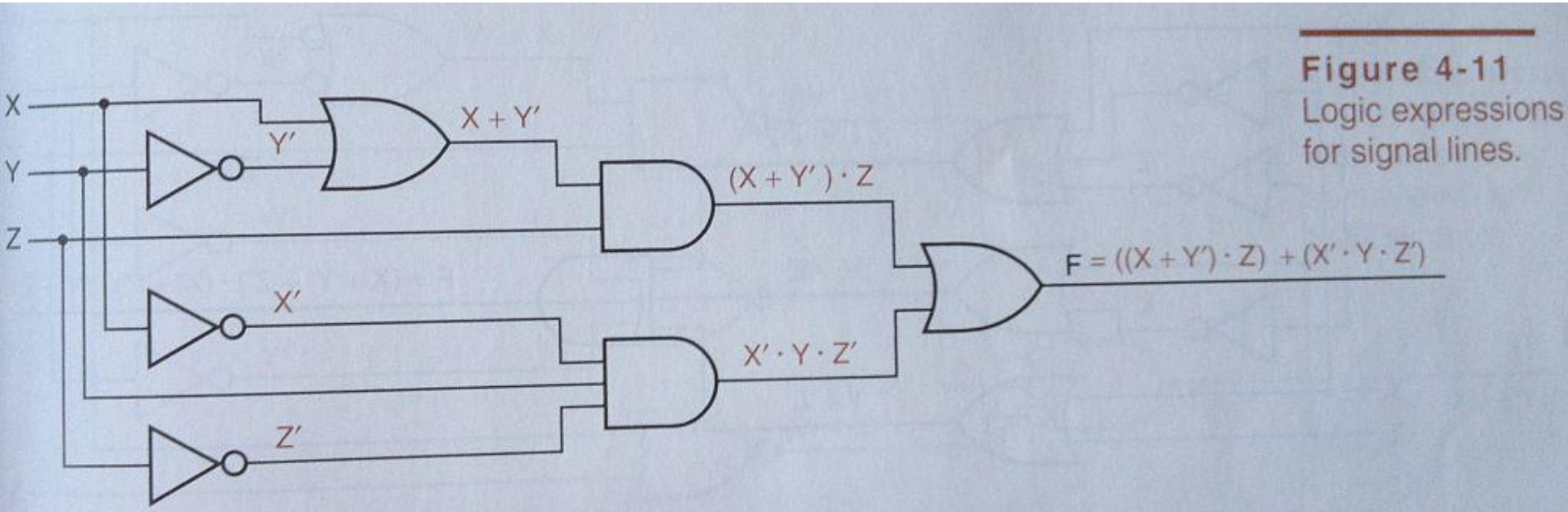

- Simplifying gives:
 - $F = X \cdot Z + Y' \cdot Z + X' \cdot Y \cdot Z'$
- **EXERCISE:** draw the new circuit!

Solution

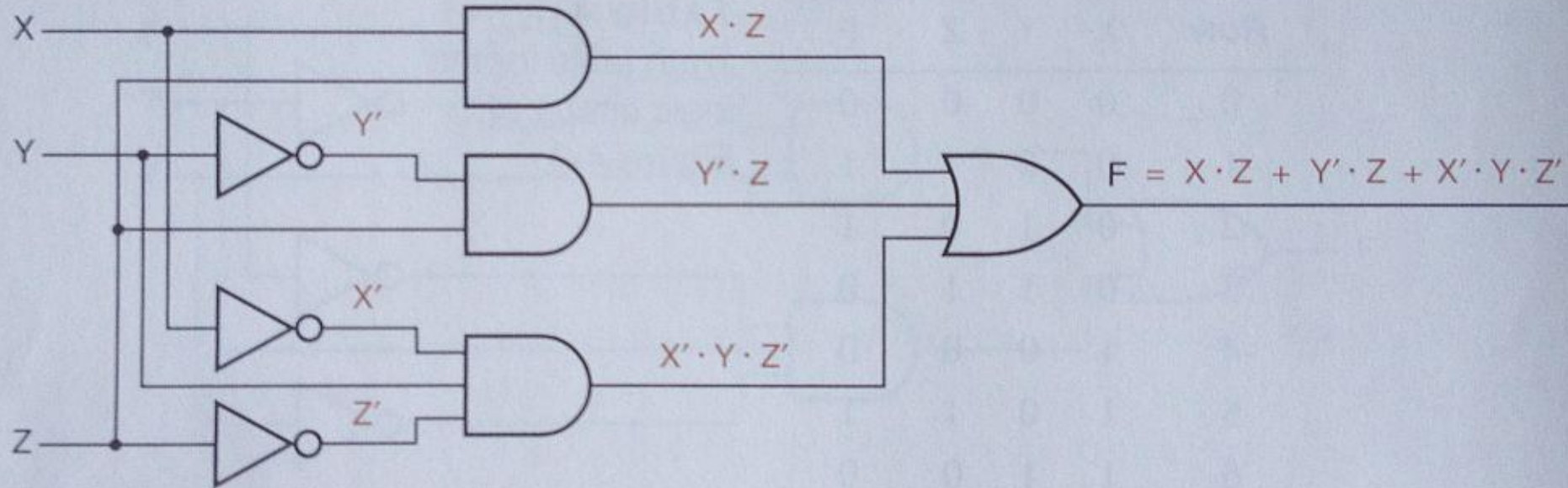


Figure 4-12 Two-level AND-OR circuit.

Another circuit

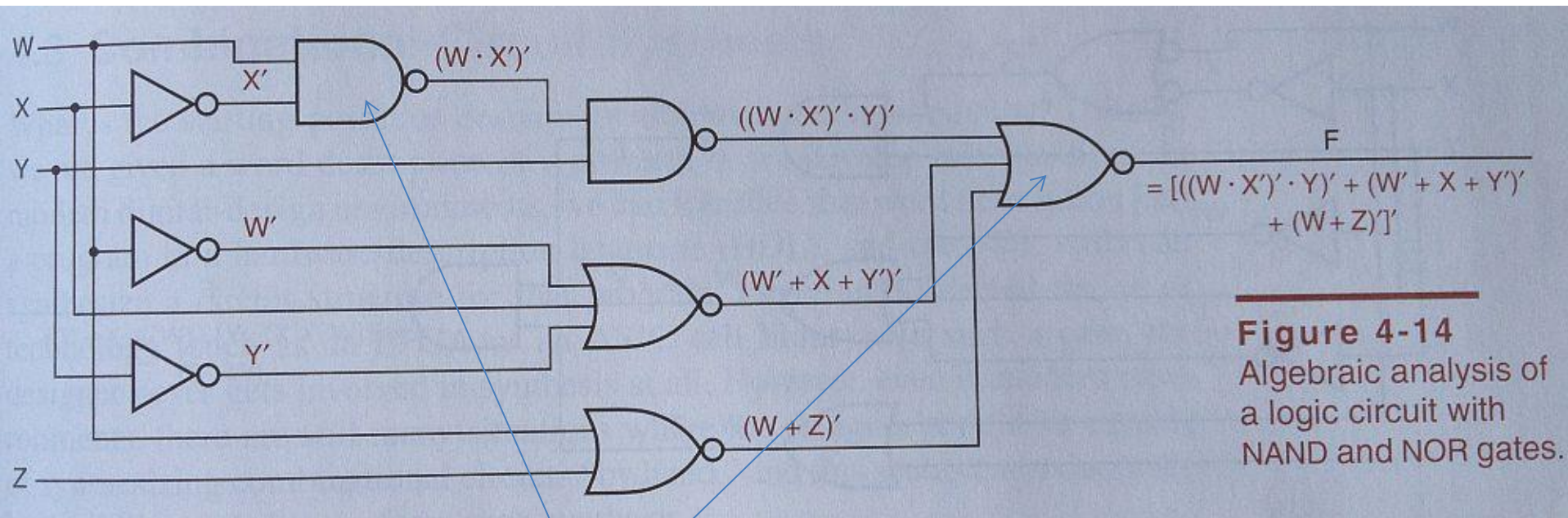


Figure 4-14

Algebraic analysis of a logic circuit with NAND and NOR gates.

- **EXERCISE:** Use DeMorgan's theorem to replace some of the blocks!

Solution

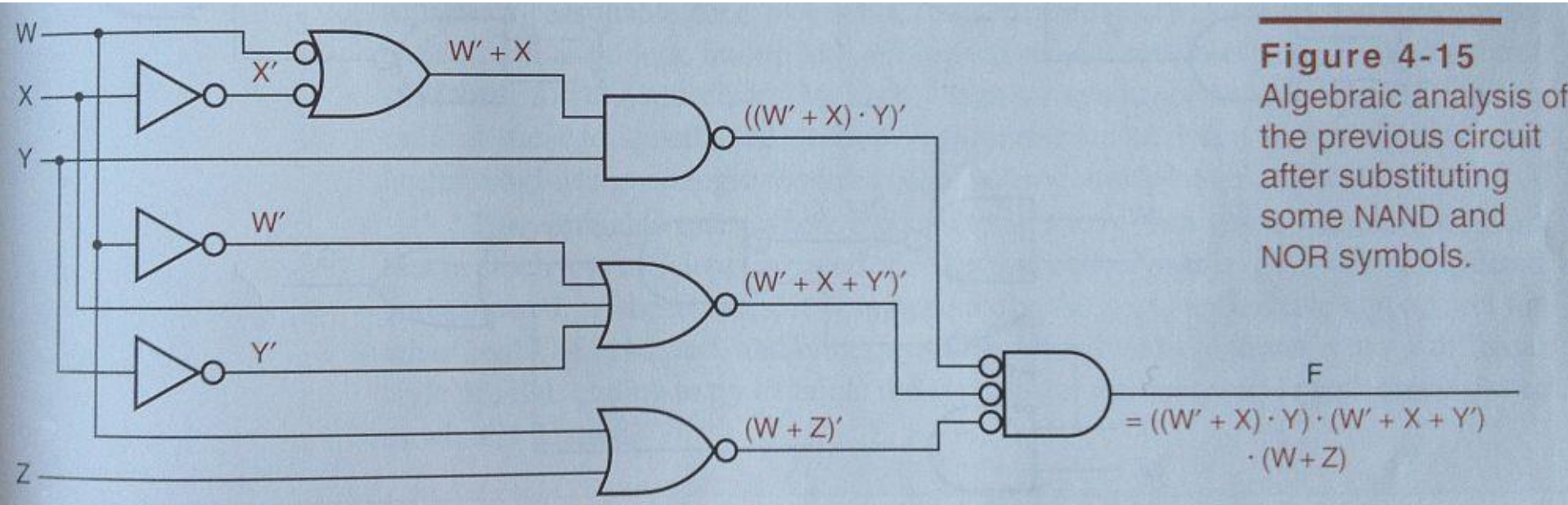


Figure 4-15
Algebraic analysis of
the previous circuit
after substituting
some NAND and
NOR symbols.

- Could this circuit be simplified even more?

Yes, remove double negations


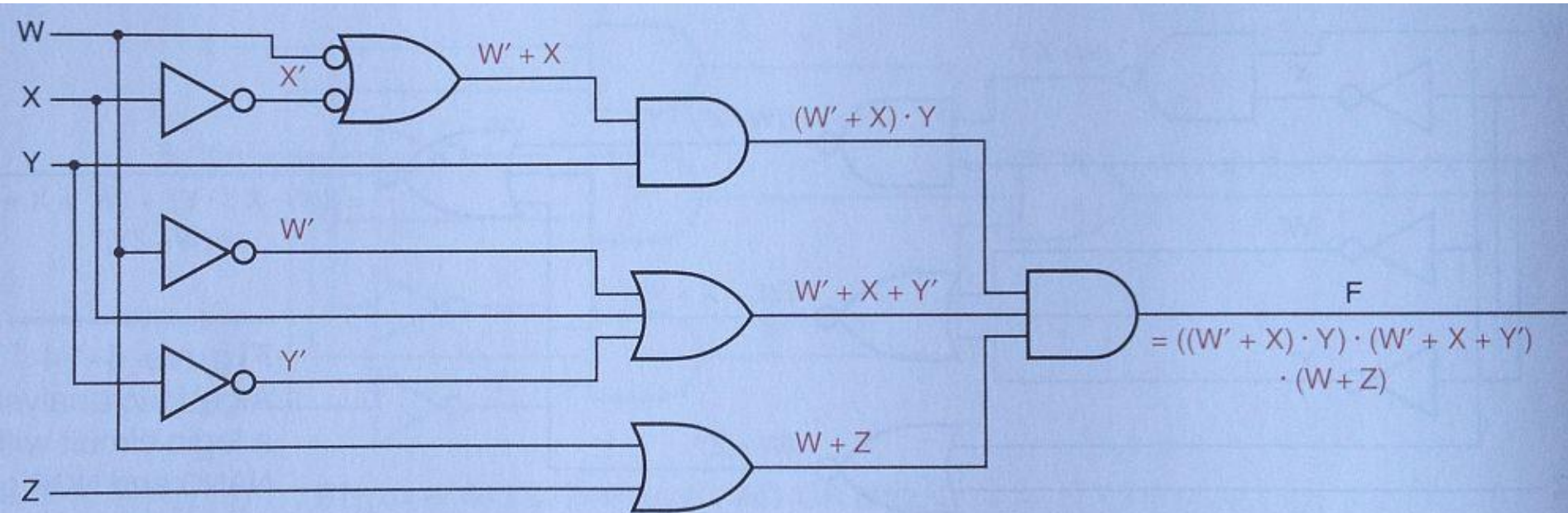


Figure 4-16 A different circuit for same logic function.

Different ways to describe the same circuit

- $G(W, X, Y, Z) = W \cdot X \cdot Y + Y \cdot Z$

Figure 4-17 Three circuits for $G(W, X, Y, Z) = W \cdot X \cdot Y + Y \cdot Z$: (a) two-level AND-OR; (b) two-level NAND-NAND; (c) with 2-input gates only.

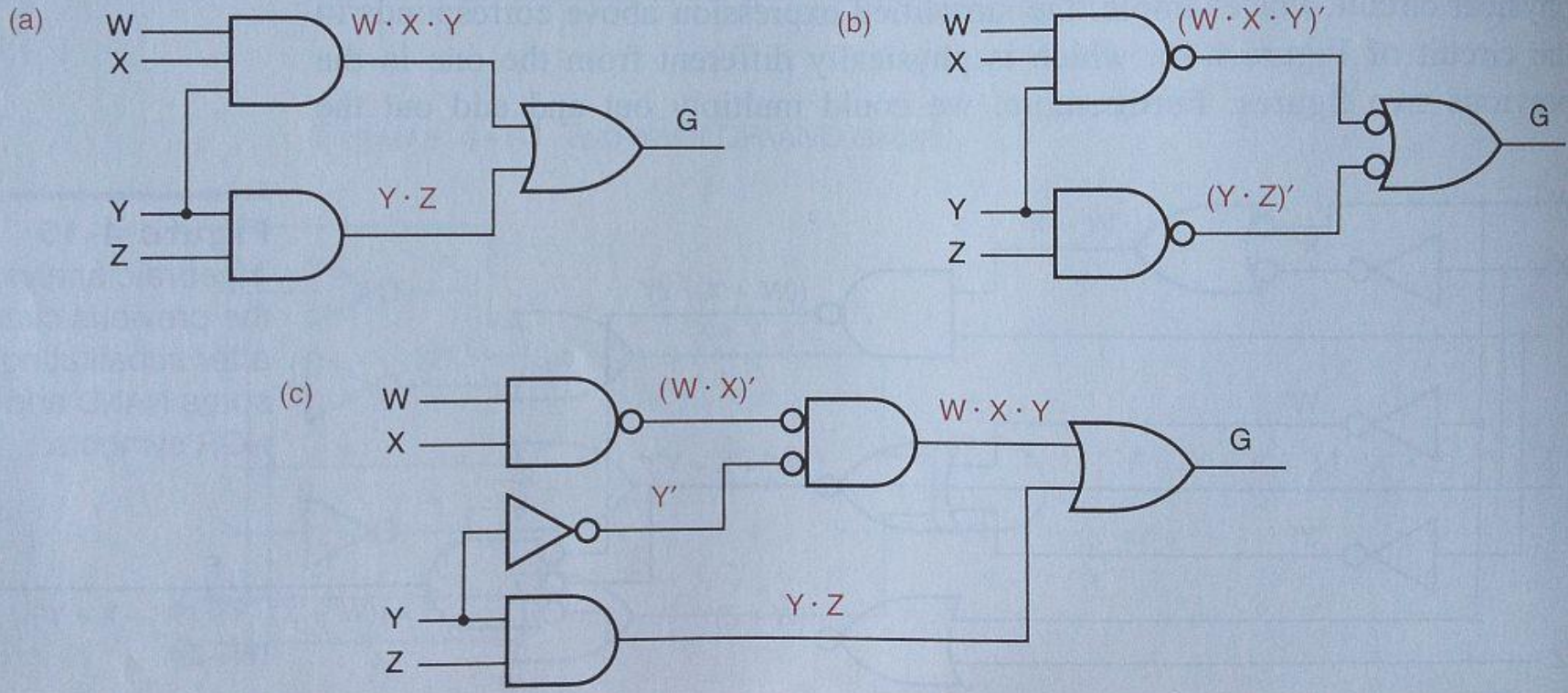

Overview of assignment 1

- Hints:
 - $A + AB = A$
 - $A + A'B = A + B$
 - $(A+B)(A+C) = A + BC$
- Other questions?