 


Embedded Systems Design, Spring 2025

Lecture 4



State machines and counters

Review from last time

- ?

State machine analysis


- States
- State machines
- Clocked synchronous state machines

- Next state logic
- Output logic

Mealy machine

- Next state = $F(\text{current state, input})$
- Output = $G(\text{current state, input})$


Figure 7-35 Clocked synchronous state-machine structure (Mealy machine).

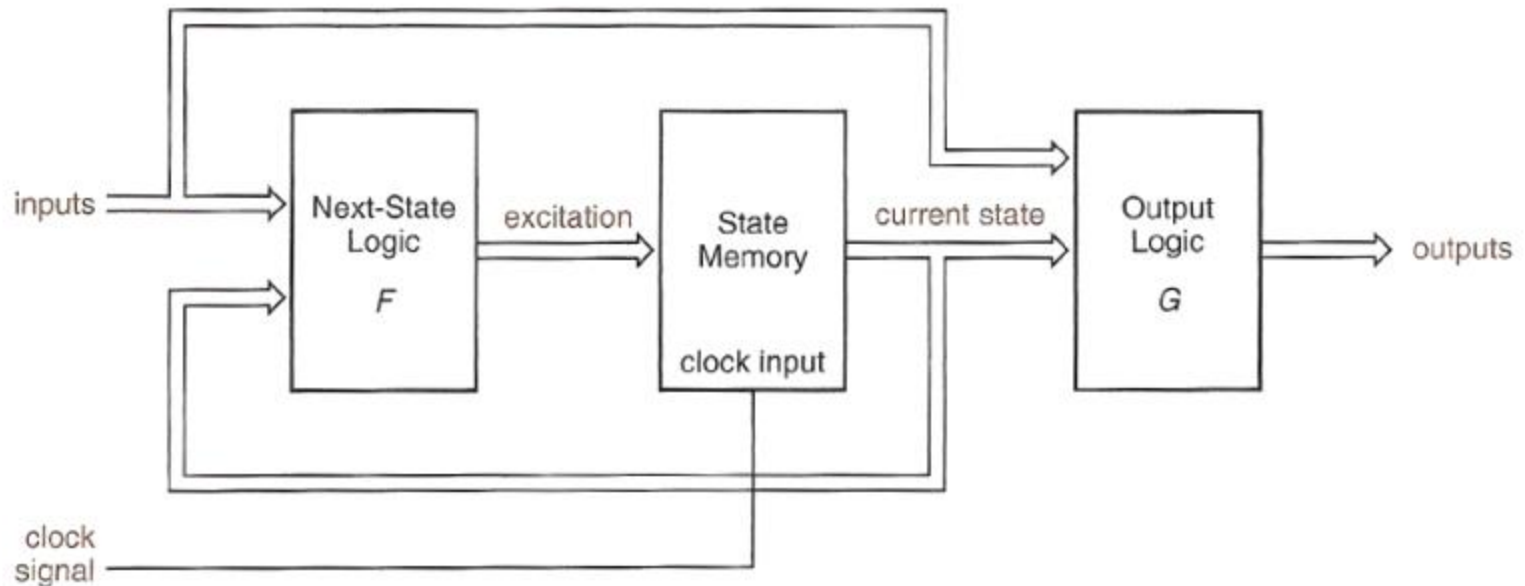

Moore Machine

- Next state = $F(\text{current state, input})$
- Output = $G(\text{current state})$

Figure 7-36 Clocked synchronous state-machine structure (Moore machine).

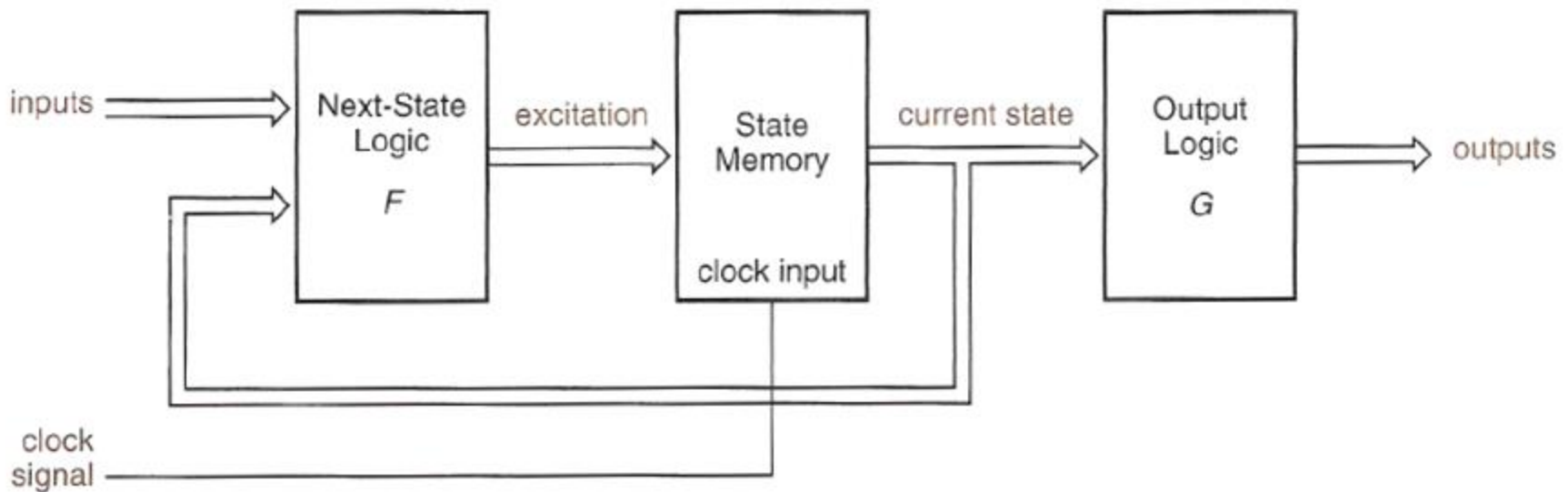

Characteristic equations

<i>Device Type</i>	<i>Characteristic Equation</i>
S-R latch	$Q^* = S + R' \cdot Q$
D latch	$Q^* = D$
Edge-triggered D flip-flop	$Q^* = D$
D flip-flop with enable	$Q^* = EN \cdot D + EN' \cdot Q$
Master/slave S-R flip-flop	$Q^* = S + R' \cdot Q$
Master/slave J-K flip-flop	$Q^* = J \cdot Q' + K' \cdot Q$
Edge-triggered J-K flip-flop	$Q^* = J \cdot Q' + K' \cdot Q$
T flip-flop	$Q^* = Q'$
T flip-flop with enable	$Q^* = EN \cdot Q' + EN' \cdot Q$

Table 7-1
Latch and flip-flop
characteristic
equations.

Example

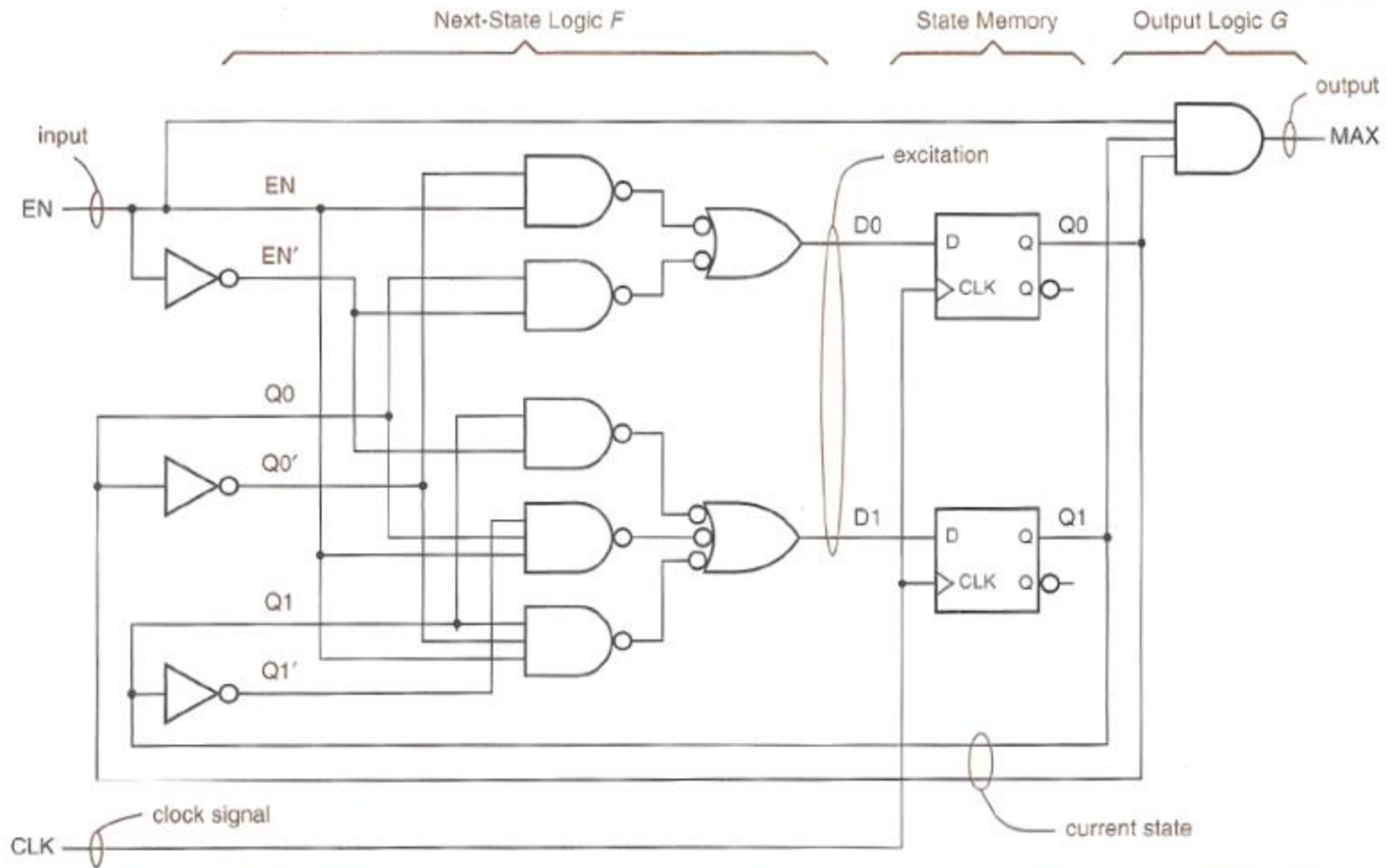


Figure 7-38 Clocked synchronous state machine using positive-edge-triggered D flip-flops.

Steps

- 1. Write the excitation equations for the FF inputs
- 2. Obtain transition equations
- 3. Determine output equations
- 4. Make transition table
- 5. Add the outputs into the transition table
- 6. Name the states and make substitutions, show the output with respect to inputs and current states
- 7. Draw state diagram

Example

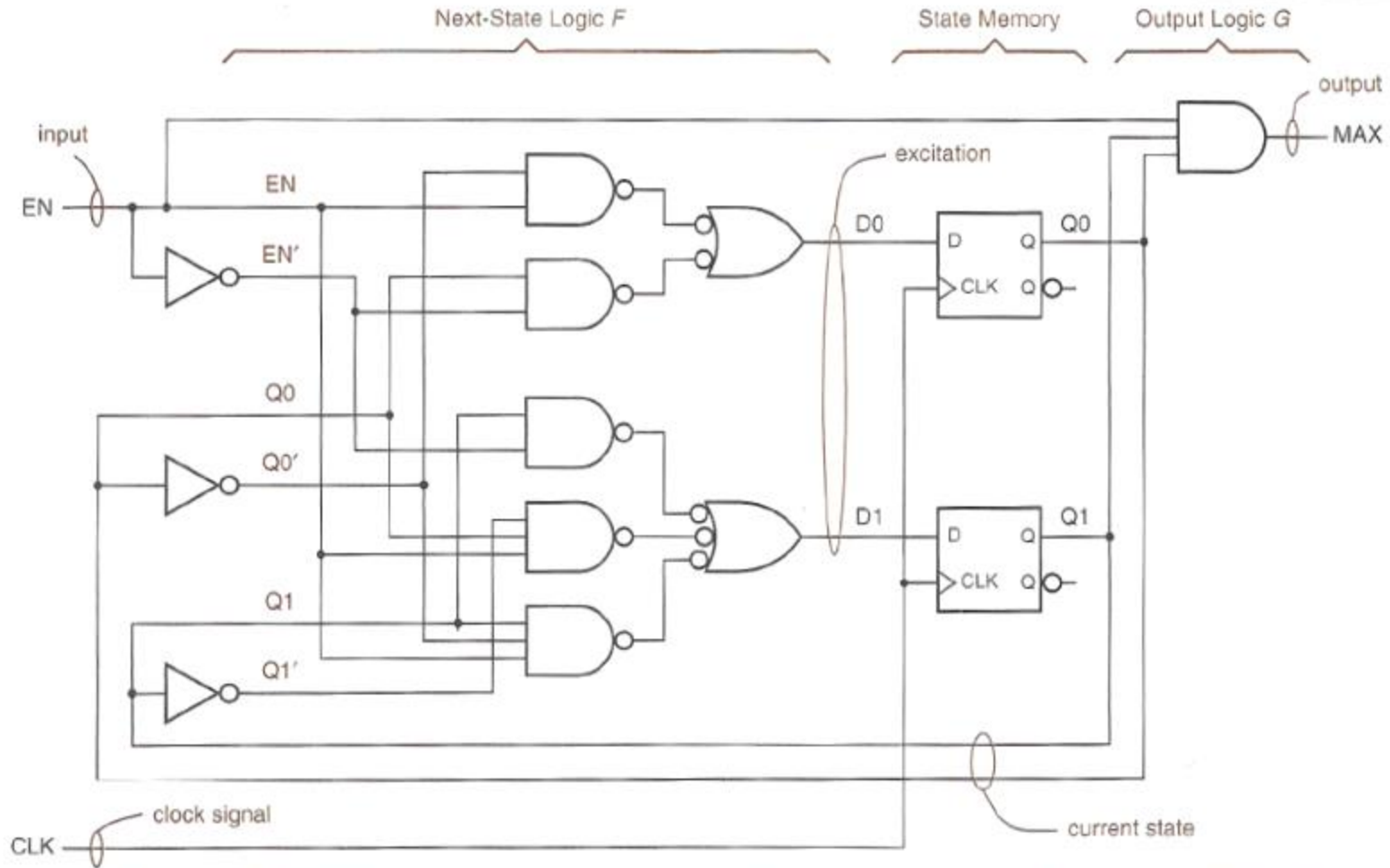


Figure 7-38 Clocked synchronous state machine using positive-edge-triggered D flip-flops.

Steps :1, 2, 3

$$D0 = Q0 \cdot EN' + Q0' \cdot EN$$

$$D1 = Q1 \cdot EN' + Q1' \cdot Q0 \cdot EN + Q1 \cdot Q0' \cdot EN$$

$$Q0^* = D0$$

$$Q1^* = D1$$

$$Q0^* = Q0 \cdot EN' + Q0' \cdot EN$$

$$Q1^* = Q1 \cdot EN' + Q1' \cdot Q0 \cdot EN + Q1 \cdot Q0' \cdot EN$$

$$MAX = Q1 \cdot Q0 \cdot EN$$

Steps 4, 5, 6

(a)

<i>Q1 Q0</i>	<i>EN</i>	
	<i>0</i>	<i>1</i>
00	00	01
01	01	10
10	10	11
11	11	00
<i>Q1* Q0*</i>		

(b)


<i>S</i>	<i>EN</i>	
	<i>0</i>	<i>1</i>
A	A	B
B	B	C
C	C	D
D	D	A
<i>S*</i>		

(c)

<i>S</i>	<i>EN</i>	
	<i>0</i>	<i>1</i>
A	A, 0	B, 0
B	B, 0	C, 0
C	C, 0	D, 0
D	D, 0	A, 1
<i>S*, MAX</i>		


Table 7-2
Transition, state, and state/output tables for the state machine in Figure 7-38.

Step 7

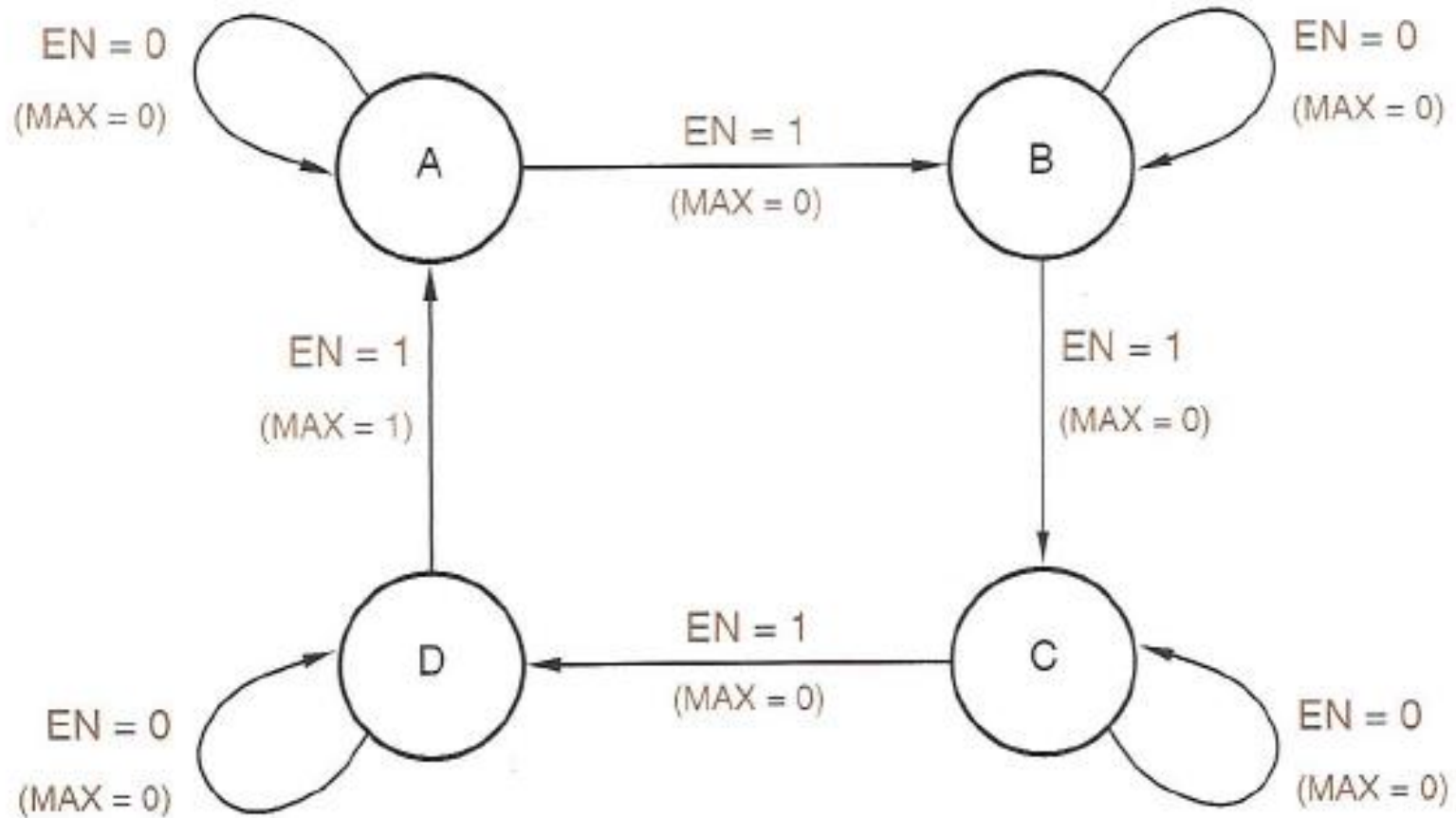


Timing diagram

Figure 7-42 Timing diagram for example state machine.

 

Same example, different circuit

Figure 7-41 Redrawn logic diagram for a clocked synchronous state machine.

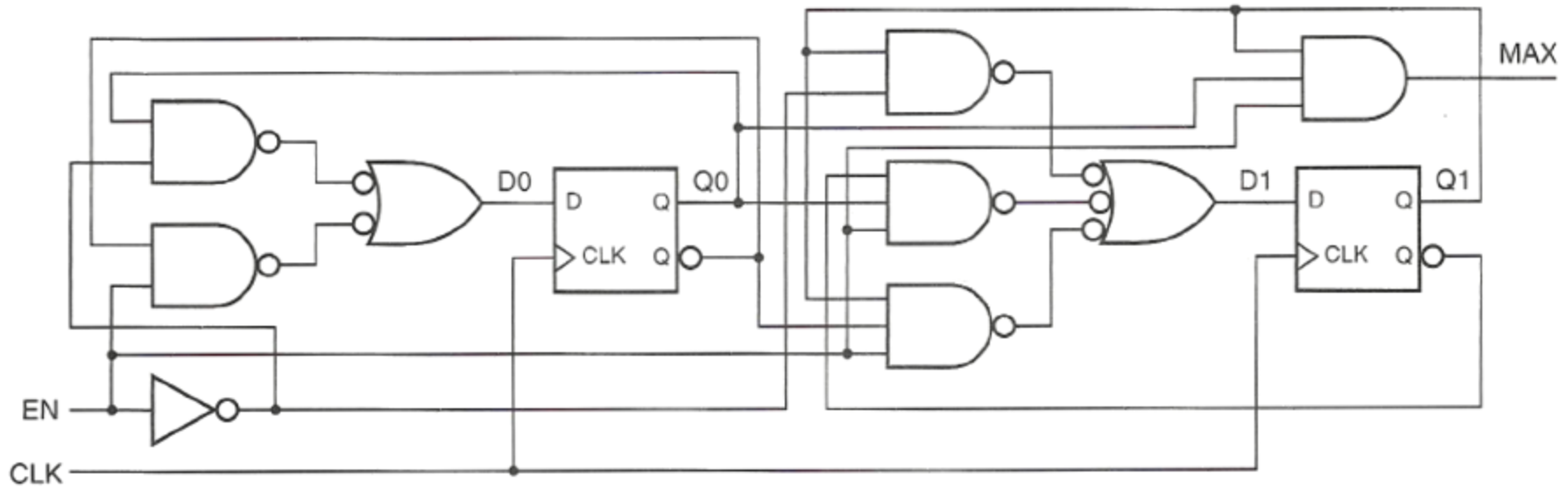


Drill state machine problem

- About 15 minutes
- Remember the steps
 - 1. Write the excitation equations for the FF inputs
 - 2. Obtain transition equations
 - 3. Determine output equations
 - 4. Make transition table
 - 5. Add the outputs into the transition table
 - 6. Name the states and make substitutions, show the output with respect to inputs and current states
 - 7. Draw state diagram

Counters

Figure 8-23
General structure
of a counter's state
diagram—a single
cycle.

 

 


Figure 7-31 Positive-edge-triggered T flip-flop: (a) logic symbol; (b) functional behavior.


 


Figure 7-32
Possible circuit designs for a T flip-flop: (a) using a D flip-flop; (b) using a J-K flip-flop.

Figure 7-33 Positive-edge-triggered T flip-flop with enable: (a) logic symbol; (b) functional behavior.

 

Ripple counter

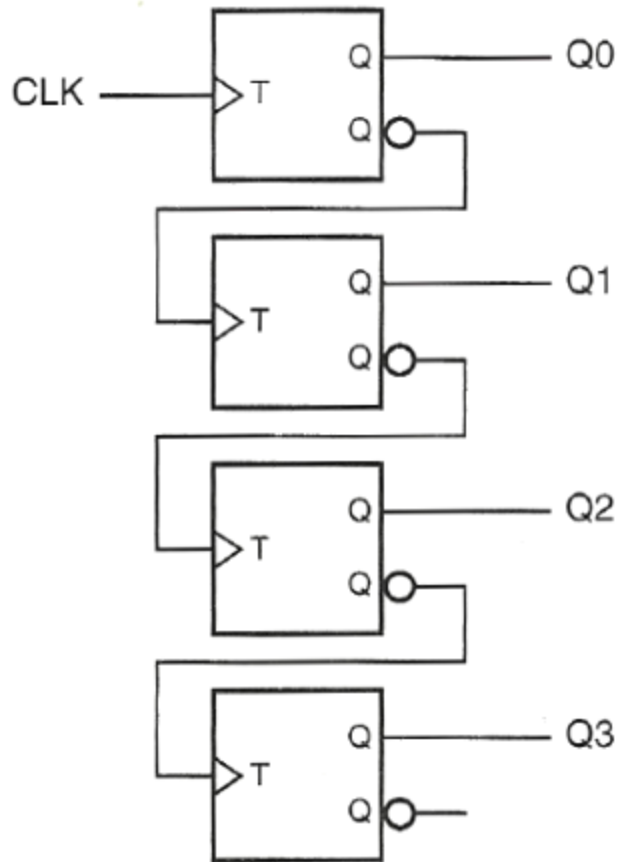


Figure 8-24
A 4-bit binary
ripple counter.

Serial enable logic

 



Figure 8-25

A synchronous 4-bit binary counter with serial enable logic.

Parallel enable logic

Figure 8-26

 A synchronous 4-bit binary counter with parallel enable logic.



Logic symbol for the 74x163 timer

 


Figure 8-27
Traditional logic
symbol for
the 74x163.

Table 8-13 State table for a 74x163 4-bit binary counter.

<i>Inputs</i>				<i>Current State</i>				<i>Next State</i>			
<i>CLR_L</i>	<i>LD_L</i>	<i>ENT</i>	<i>ENP</i>	<i>QD</i>	<i>QC</i>	<i>QB</i>	<i>QA</i>	<i>QD*</i>	<i>QC*</i>	<i>QB*</i>	<i>QA*</i>
0	x	x	x	x	x	x	x	0	0	0	0
1	0	x	x	x	x	x	x	D	C	B	A
1	1	0	x	x	x	x	x	QD	QC	QB	QA
1	1	x	0	x	x	x	x	QD	QC	QB	QA
1	1	1	1	0	0	0	0	0	0	0	1
1	1	1	1	0	0	0	1	0	0	1	0
1	1	1	1	0	0	1	0	0	0	1	1
1	1	1	1	0	0	1	1	0	1	0	0
1	1	1	1	0	1	0	0	0	1	0	1
1	1	1	1	0	1	0	1	0	1	1	0
1	1	1	1	0	1	1	0	0	1	1	1
1	1	1	1	0	1	1	1	1	0	0	0
1	1	1	1	1	0	0	0	1	0	0	1
1	1	1	1	1	0	0	1	1	0	1	0
1	1	1	1	1	0	1	0	1	0	1	1
1	1	1	1	1	0	1	1	1	1	0	0
1	1	1	1	1	1	0	0	1	1	0	1
1	1	1	1	1	1	0	1	1	1	1	0
1	1	1	1	1	1	1	0	1	1	1	1
1	1	1	1	1	1	1	1	0	0	0	0


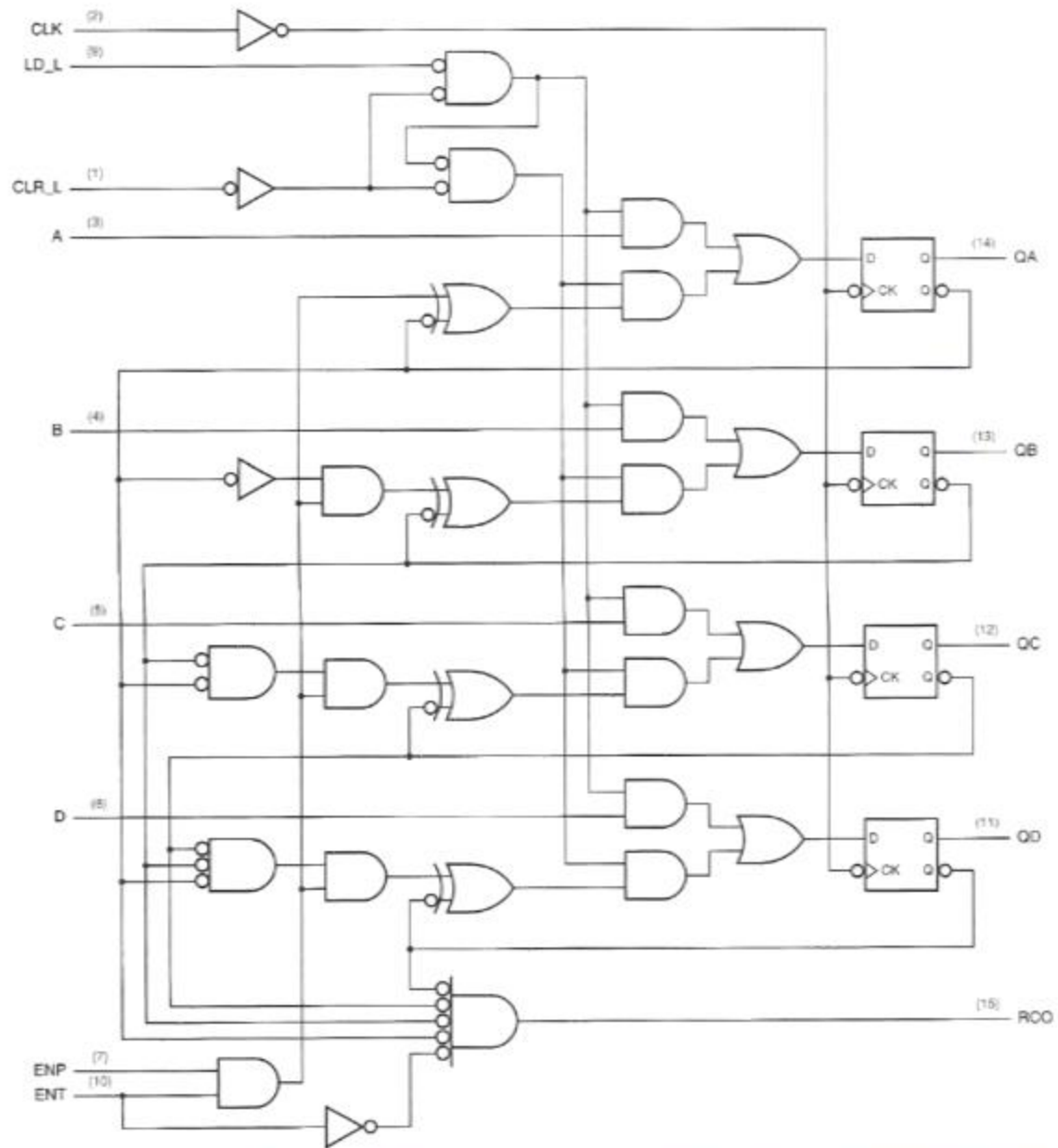


Figure 8-28 Logic diagram for the 74x163 synchronous 4-bit binary counter, including pin numbers for a standard 16-pin DIP package.

Divide by 16 counter

Figure 8-30 Clock and output waveforms for a free-running divide-by-16 counter.

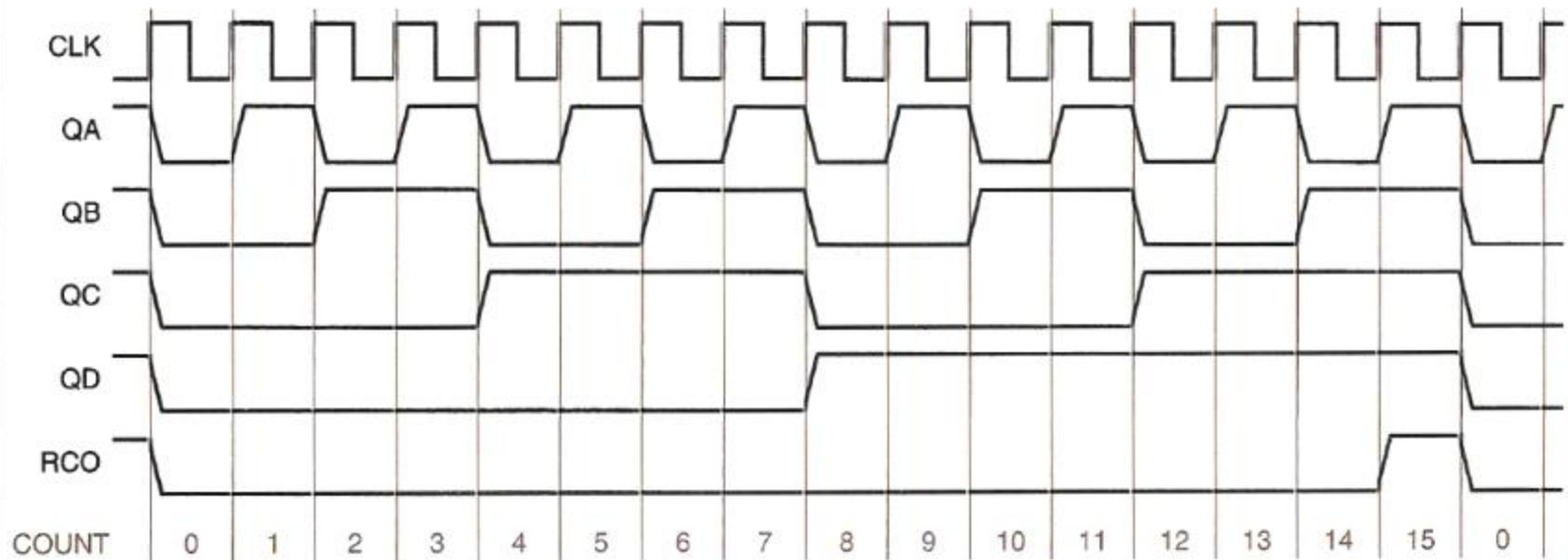

Example of binary counter

- <https://www.youtube.com/watch?v=U7ARbuAPPs4>
- **Task:** simulate a 4 bit counter using the following template
- <https://simulator.io/board/lrBpIXomS7/229>

Assignment 2

- ...discussion